

Roll no. \_\_\_\_\_

ID: 188422

**Semester: Level 3, Sem II**

**Branch: DVOC (Ref. & Air Cond., Medical Imaging Tech., Auto. Servicing, ITM, PT, SD, AMT, FP, EMS)**

**Subject Name: Basic Electricity**

**Time Allowed : 2 Hrs.**

**MM:50**

**Section –A**

**Note: Multiple Choice questions. All questions are compulsory.**

**5x1=5**

- Q.1 Filament of a bulb is made up of:  
a. Copper                      b. Iron                      c. Zinc                      d. Tungsten
- Q.2 L in LED stands for:  
a. Lamp                      b. Light                      c. Lite                      d. Lower
- Q.3 Capacitor is used to store \_\_\_\_:  
a. Charge                      b. Power                      c. Current                      d. Resistance
- Q.4 When two capacitors of capacitance C are connected in parallel, effective capacitance will be:  
a. C/2                      b. C                      c. 2C                      d. 4C
- Q.5 Value of power factor lies between:  
a. 0, 2                      b. 0,1                      c. 1, 2                      d. -1, 1

**Section-B**

**Note: Objective type questions. All questions are compulsory.**

**5x1=5**

- Q.6 Define power factor?
- Q.7 What is r.m.s. value?
- Q.8 Tube light is used to convert electrical energy into light. (True/False)
- Q.9 Battery is used to store DC. (True/False)
- Q.10 Define Q-Factor?

**Section –C**

**Note: Short answer type Questions. Attempt any six questions out of eight questions.**

**6x5=30**

- Q.11 Differentiate between AC and DC.
- Q.12 Explain Kirchhoff's law with suitable diagram and mathematical expression?
- Q.13 List any five differences between primary and secondary cell?
- Q.14 Define: Frequency, Peak Value, Form Factor, Capacitance, Phase Difference
- Q.15 Explain Faraday's laws of electromagnetic induction?
- Q.16 Derive the equation for energy stored in an inductor?
- Q.17 Explain the concept of force acting on current carrying conductor placed in magnetic field?
- Q.18 Explain ohm's law? Give its limitations?

**Section D**

**Note: Long answer questions. Attempt any one questions out of two questions.**

**1x10=10**

- Q.19 Define resistance? List factors on which resistance of a material depends? Derive an equation for effective resistance of two resistor connected in series and parallel?
- Q.20 Draw and explain R-L-C series circuit?