

No. of Printed Pages : 4
Roll No.

181031/171031/
121031/031031

**3rd Sem / Eltx, Mechatronics,
Med. Eltx, Power Eltx, Elect. & Eltx. Engg.**

**Subject:- Electronic Devices and circuits /
Analog Eltx. II**

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

Q.1 PUSH PULL amplifier use:

- a) Class A b) Class B
- c) Class C d) All

Q.2 An OP-AMP has following number of input terminal

- a) 1 b) 2
- c) 3 d) 4

Q.3 Transistor can be used as _____ for application

- a) Switch b) amplifier
- c) inverter d) All

Q.4 IC 555 Timer can be used as _____

- a) Monostable b) Astable
- c) both d) None

Q.5 In class A Amplifier, collector current flows for _____

- a) Less than half cycle b) Half the cycle
- c) Full cycle d) Less than entire cycle

(1)

181031/171031/
121031/031031

Q.6 Transformer coupling is an example of _____

- a) Direct coupling b) AC coupling
- c) Impedance coupling d) None

Q.7 An oscillator always needs an amplifier with _____

- a) Negative feedback b) Positive feedback
- c) Both feedback d) LC tank circuit

Q.8 555 timer consists of _____

- a) Comparator
- b) RS flip flop
- c) Transistor and resistor
- d) All above

Q.9 For an ideal OP AMP, value of term CMRR is _____

- a) zero b) infinite
- c) 100 d) none

Q.10 A tuned voltage amplifier is used to amplify signal of _____

- a) low frequency b) medium frequency
- c) high frequency d) none of the above

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

Q.11 SMPS stands for _____

Q.12 OPAMP has _____ number of inputs.

(2)

181031/171031/
121031/031031

- Q.13 A common device which can be used as an electronic switch is a _____
- Q.14 Define CMRR.
- Q.15 In resonant circuit, at resonance, net reactance is zero. (True/False)
- Q.16 To generate square wave _____ multivibrator is used.
- Q.17 What is power amplifier?
- Q.18 The amplitude of _____ oscillations decreases with time.
- Q.19 Positive feedback _____ bandwidth.
- Q.20 The output waveform of 555 timer is _____.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain the working of RC phase shift oscillator.
- Q.22 Explain block diagram of IC 555.
- Q.23 Explain in brief operation of DC coupled amplifier and its frequency response.
- Q.24 Discuss the effect of negative feedback on stability and bandwidth of an amplifier.
- Q.25 Explain the gain of an amplifier.
- Q.26 Explain working of Class A amplifier.
- Q.27 Explain difference between voltage and power amplifiers.

(3) 181031/171031/
121031/031031

- Q.28 Explain series resonant circuit and bandwidth of resonant circuit.
- Q.29 Define
a) Collector efficiency and distortion
b) Heat dissipation curve
- Q.30 Explain working of monostable multivibrator.
- Q.31 Explain the working of IC 7905.
- Q.32 What are types of feedback? Explain in brief.
- Q.33 Explain load regulation.
- Q.34 Explain characteristics of ideal OP AMP and its block diagram.
- Q.35 Explain the working of Single tuned amplifier.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain OP AMP as inverter, scale changer, integrator & differentiator.
- Q.37 Explain RC coupled amplifier with bypass capacitor.
- Q.38 Explain complementary symmetry Push pull amplifier in detail and its advantages over PUSH PULL amplifier.

(1380) (4) 181031/171031/
121031/031031