

- Q.32 Explain RL as integrator circuits.
- Q.33 What are essentials of oscillator?
- Q.34 What is effect of removing by pass capacitor from CE transistor amplifier.
- Q.35 Explain impedance matching in amplifiers

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain various diode clipping circuits
- Q.37 Explain block diagram and working of 555 timer.
- Q.38 Explain working of Push Pull amplifier & its advantages and disadvantages

No. of Printed Pages : 4
Roll No.

120943

4th Sem / Elect, Power Station Engg., Elect. & Eltx. Engg. Subject:- Electronics - II

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 Complementary PUSH PULL amplifier uses:
- Class A
 - Class B
 - Class C
 - None
- Q.2 The material with a piezo electric effect is:
- Quartz
 - Silicon
 - GaAs
 - Rochelle salt
- Q.3 Emitter bypass capacitor _____ gain of an amplifier
- Increases
 - Decreases
 - Makes zero
 - Makes 1
- Q.4 Amplifiers uses _____ feedback
- Positive
 - Negative
 - Sinusoidal
 - None
- Q.5 Transformer coupling is an example of _____
- Direct coupling
 - AC coupling
 - DC coupling
 - Impedance coupling

- Q.6 When ambient temperature increases, the power rating of transistor _____:
- a) Decreases b) Increases
c) Remain same d) None
- Q.7 The collector efficiency of amplifier is maximum for:
- a) Class A b) Class B
c) Class C d) Class AB
- Q.8 A clamper circuit is known as:
- a) Average circuit b) Dc resistor
c) Ac resistor d) Inverter
- Q.9 Output waveform of 555 timer is:
- a) Sine b) triangular
c) Rectangular d) Elliptical
- Q.10 A transistor can be used as _____ for application
- a) Amplifier b) Inverter
c) Switch d) All

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Define dissipation capability?
- Q.12 Define voltage gain?
- Q.13 What is heat sink in amplifiers?
- Q.14 What is an Oscillator

- Q.15 What is feedback.
- Q.16 What is voltage amplifier?
- Q.17 What are clamping circuits?
- Q.18 Define CVT.
- Q.19 What is offset voltage?
- Q.20 Two advantages of negative feedback.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 What is difference between oscillator and alternator.
- Q.22 How transistor works as a switch.
- Q.23 Explain working principle of IC voltage regulator.
- Q.24 Explain double tuned voltage amplifier.
- Q.25 Explain working of class A amplifier in brief with input and output waveforms.
- Q.26 Explain working of wien bridge oscillator.
- Q.27 Discuss the working principle of astable multivibrator.
- Q.28 Explain Emitter follower circuit and its applications?
- Q.29 What is advantage of voltage IC regulator over other regulators.
- Q.30 What do you mean by offset even voltages and currents?
- Q.31 Explain RC as differentiator circuits.