

- c) 7 d) 8
- Q.6 Which device has more operating speed.
a) LED b) LCD
c) None of these
- Q.7 Which logic family is the fastest.
a) RTL b) DTL
c) ECL d) TTL
- Q.8 IC 74237 is a _____.
a) 1:16 Demux b) 1:8 Demux
c) 16:1 mux d) 8:1 mux
- Q.9 The process of converting a known input digit into a coded output is known as.
a) Decoding b) Encoding
c) Multiplexing d) None of these
- Q.10 The base of a hexadecimal number system is _____.
a) 15 b) 17
c) 16 d) 14

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Digital signals are used in DBMS in Banks. True/False
- Q.12 The base or radix of a decimal number is _____.

- Q.13 Draw symbol of OR gate.
- Q.14 Excess-3 code is a non-weighted code. True/False
- Q.15 Logical inversion is also known as NOT operation. True/False
- Q.16 _____ is the example of sequential circuits.
- Q.17 2:1 mux has only two select lines. True/False
- Q.18 Flip flop have clock input. True/False
- Q.19 Counter are used in automobile parking. True/False
- Q.20 A/D convertor is used in digital voltmeters. True/False

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Differentiate between analog system and digital systems.
- Q.22 Divide $(1111000)_2$ by $(100)_2$
- Q.23 What do you mean by error detecting codes.
- Q.24 Implement a NOR gate by using NAND gates only.
- Q.25 State and explain De Morgan's theorems
- Q.26 Explain half adder with its truth table & logical diagram.
- Q.27 Explain the term multiplexer. Design a 2:1 multiplexer.