

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Describe capacitors and their types, also discuss their series and parallel connection.
- Q.24 Draw and explain Delta connection for three phase supply, also discuss Delta to Star conversion.
- Q.25 State and explain the Laws of electro-magnetic induction.

No. of Printed Pages : 4
Roll No.

221521

2nd Sem. / Instrumentation and Control Engg.

Subject : Fundamentals of Electrical Engg.

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

- Q.1 Unit of Voltage is _____.
a) Amperes b) Volts
c) Watt d) None of these
- Q.2 An instrument that measures the current is known as _____.
a) Ohm water b) Voltmeter
c) Ammeter d) Wattmeter.
- Q.3 Unit of Resistivity is _____.
a) Ω b) Ωm
c) Amperes d) Volts

- Q.4 An Ideal Voltage source has _____.
- Zero internal Resistance
 - Infinite internal Resistance
 - High internal Resistance
 - very low internal Resistance
- Q.5 SI unit of magnetic flux density is _____.
- Tesla
 - Weber
 - Ampere
 - None of these
- Q.6 A tuned circuit uses _____
- R-L
 - R-C
 - L-C at its components
 - XL-C

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 Define secondary cell.
- Q.8 Mention one application of Lead acid battery.

(2)

221521

- Q.9 The parallel resonance magnifies the current in the circuits. (True/False)
- Q.10 Define DC.
- Q.11 The term power factor comes into the picture in Ac circuits only. (True/False)
- Q.12 Explain KVL.

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Write a short note on Lithium -ion battery.
- Q.14 What is Magnetic circuit.
- Q.15 Draw and explain R-C series circuit with its phasor diagram.
- Q.16 State and Explain Norton Theorem.
- Q.17 Write the factors affecting Resistance of a Resistor.
- Q.18 State laws of Resistance.
- Q.19 Explain Kirchoff's current law.
- Q.20 Write a short note on admittance and impedance.
- Q.21 Write a short note on Solar panels.
- Q.22 Discuss Self and Mutual inductance.

(3)

221521