

- b) Multi stage Voltage amplifier
- c) Power Amplifier
- d) All of these

Q.4 The base value of Octal No. System is_____

- a) 2 b) 4
- c) 8 d) 10

Q.5 A byte represents _____.

- a) 3 nibble b) 8 nibble
- c) 2 nibble d) 4 nibble

Q.6 D Flip Flop is_____ Flip Flop.

- a) Delayed b) Digital
- c) Differential d) Dial type

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 Expand PIPO.
- Q.8 Draw Symbol of OR Gate.
- Q.9 Expand MOSFET.

Q.10 A transistor contains _____ PN junction.

Q.11 Define Ripple.

Q.12 Mention name of any one A/D convertor.

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

Q.13 Write a short note on PN junction Diode.

Q.14 Discuss Structure of PNP Transistor.

Q.15 Explain NOT and AND Gate with their symbol and truth table.

Q.16 Write a short note on combinational Circuits.

Q.17 Differentiate between Analog and digital signals.

Q.18 Discuss I/P and O/P connections of CB configuration.

Q.19 Explain Diode as a Half wave rectifier.

Q.20 Describe characteristics and applications of Zener Diode.

Q.21 Differentiate between JFET and BJT.