

No. of Printed Pages : 4
Roll No.

220953

5th Sem / Electrical , IC

Subject : Industrial Electronics and Control of Drives

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

- Q.1 A TRIAC is a _____ switch (CO1)
a) Unidirectional b) Mechanical
c) Bidirectional d) Four directional
- Q.2 The SCR is turned off when the anode current falls below (CO1)
a) Break over voltage
b) Forward current rating
c) Latching current
d) Holding current
- Q.3 A cycloconverter is a (CO3)
a) One stage power converter
b) One stage voltage converter
c) One stage frequency converter
d) None of the above

(1)

220953

- Q.4 If firing angle of an SCR decreases, the output is (CO2)
a) Increased b) Decreased
c) Maximum d) Remain unaffected

- Q.5 Which method is used to control the speed of DC shunt motor above normal speed? (CO4)
a) Armature voltage control method
b) Flux control method
c) Both option (a) & (b)
d) None of the above

- Q.6 UPS stands for (CO5)
a) Unipolar Power Supply
b) Uninterrupted polar Supply
c) Uninterrupted Power Supply
d) None of the above

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 Name any two members of the thyristor family. (CO1)
- Q.8 Define chopper. (CO3)
- Q.9 What is an Electric Drive? (CO4)

(2)

220953

- Q.10 Expand SMPS. (CO5)
- Q.11 Define Commutation. (CO1)
- Q.12 Define Controller Rectifier. (CO2)

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Draw symbol and V-I characteristics of DIAC. (CO1)
- Q.14 Explain the different methods of triggering of an SCR. (CO1)
- Q.15 Explain UJT as a Relaxation oscillator. (CO1)
- Q.16 Difference between on -line UPS and off-line UPS. (CO5)
- Q.17 What is step down chopper? Explain its working. (CO3)
- Q.18 Explain the working of single phase half wave controlled rectifier with resistive Inductive (R-L) Load with proper circuit diagram and voltage current waveforms.
- Q.19 Explain single-phase full-controlled full wave rectifier. (CO2)
- Q.20 What do you mean by inverter? What are its different applications? (CO3)

(3)

220953

- Q.21 Draw and explain the Block Diagram of an Electric Drive. (CO4)
- Q.22 Draw Block Diagram of SMPS. (Co5)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Explain the construction, working principle, and V-I characteristics of SCR. (CO1)
- Q.24 Explain the working principle of single-phase to single-phase cycloconverter. (CO3)
- Q.25 Write a short note on any two:
- a) Heat sink for thyristor (CO1)
 - b) Power converter for electric vehicle charging. (CO5)
 - c) Concept of freewheeling diode. (CO2)

(1780)

(4)

220953