

- Q.26 Write any five instructions for maintenance and care of lead acid batteries.
- Q.27 Compare two modes of dual converter.
- Q.28 Differentiate between holding current and latching current of a thyristor.
- Q.29 Give the principle of operation of HVDC Transmission.
- Q.30 What are AC and DC drivers?
- Q.31 Explain any five methods of triggering SCR.
- Q.32 Explain the operation of Dual Converter in non-Circulating mode.
- Q.33 Give the symbol of TRIAC. What is the working principle of TRIAC.
- Q.34 Write a short note on Electric drivers.
- Q.35 Write merits and demerits of Series Inverter.

Section-D

Note: Long answer questions. Attempt any two question out of three Questions. (2x10=20)

- Q.36 Define construction of SCR with a diagram. Explain working principle and modes of operation of SCR.
- Q.37 Explain the working of Single-phase full wave Center-Tapped and bridge Rectifiers with circuit diagram.
- Q.38 Write a note on
- DV/DT protection
 - Online inverter
 - SMPS

No. of Printed Pages : 4

120953/030953/105853

Roll No.

5th Sem.

Branch : Elect, Power Station Engg., Elect. & Eltx. Engg.

Subject : Industrial Electronics & Control of Drives

Time : 3 Hrs.

M.M : 100

SECTION-A

Note: Multiple choice Questions. All Questions are compulsory. (10x1=10)

- Q.1 MOSFET is a
- Current controlled device
 - Voltage controlled device
 - Both A & B
 - Power controlled device
- Q.2 A TRIAC is a _____ Switch.
- Bidirectional
 - Unidirectional
 - Omnidirectional
 - Mechanical
- Q.3 A cyclo - Converter is _____ converter
- AC to DC
 - DC to DC
 - AC to AC
 - DC to AC
- Q.4 A free wheeling diode is used in a controlled rectifiers circuit is case of
- Capacitive load
 - Inductive load
 - Resistive load
 - All types of load

- Q.5 ADIAC is used to
- Commutate a triac
 - Trigger a triac
 - A protect a triac
 - None
- Q.6 In rectifiers, load current flow is
- Unidirectional
 - Bidirectional
 - Non directional
 - Either A or B
- Q.7 _____ can be used as a DC static switch
- GTO
 - Transistor
 - Both GTO & Transistor
 - TRIAC
- Q.8 SMPS are based on the _____ principle.
- Phase control
 - Integral control
 - Chopper
 - MOSFET
- Q.9 An inverter converts
- DC into variable DC
 - AC into DC
 - DC into AC
 - AC into AC with different frequency
- Q.10 The duty cycle of a chopper is given by
- $\frac{T_{on}}{T_{off}}$
 - $\frac{T_{off}}{T_{on}}$
 - $\frac{T_{off}}{T_{on}+T_{off}}$
 - $\frac{T_{on}}{T_{on}+T_{off}}$

Section-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 For wide range speed control _____ drives are used.
- Q.12 In half wave rectifiers, one switching device is used. (True/False)
- Q.13 The full form of UPS is _____.
- Q.14 Draw symbol of DIAC.
- Q.15 A UJT has _____ PN junction.
- Q.16 The value of latching current is more than Holding Current. (True/False)
- Q.17 A rectifier converter _____ to _____.
- Q.18 What is Firing angle?
- Q.19 What is slip power?
- Q.20 Name any two types of commonly used batteries.

Section-C

Note: Short answer type Question. Attempt any twelve questions out of fifteen Questions. (12x5=60)

- Q.21 Differentiate between step-up and step down chopper.
- Q.22 What is UPS? What are the applications of the UPS system?
- Q.23 Explain about constant V/F operation.
- Q.24 Differentiate between controlled and uncontrolled rectifiers.
- Q.25 Show basic construction of a UJT. What is its intrinsic standoff ratio?