

No. of Printed Pages : 4

120955/30955/105855

Roll No.

5th Sem / Branch: Elect, GE, power station Engg.

Subject:- Digital Electronics and Microprocessors

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 Every rational number is a -
a) Whole number b) Real number
c) Natural number d) None of the above
- Q.2 The only function of NOT gate is to
a) Stop signal
b) Invert input signal
c) Act as a universal gate
d) None of the above
- Q.3 In Boolean algebra, the bar sign (-) indicates.....
a) OR operation b) AND operation
c) NOT operation d) None of the above
- Q.4 A _____ value is represented by a Boolean expression.
a) Positive b) Recursive
c) Negative d) Boolean
- Q.5 What is the function of an enable input on a multiplexer chip?
a) To apply Vcc
b) To connect ground

(1) 120955/30955/105855

- c) To active the entire chip
d) To active one half of the chip

Q.6 In J-K flip-flop, the function $K=J$ is used to realize

- a) D flip-flop b) S-R flip-flop
c) T flip-flop d) S-K flip-flop

Q.7 How many control lines are present in analog to digital converter in addition to reference voltage?

- a) Three b) Two
c) One d) None of the above

Q.8 Disk and tapes are type of

- a) Serial memory
b) Combinational memory
c) State memory
d) Flip-flop

Q.9 In 8085, 16-bit address bus, which can address upto?

- a) 16KB b) 32KB
c) 64KB d) 128KB

Q.10 There are _____ general purpose registers in 8085 processor.

- a) 5 b) 6
c) 7 d) 8

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

Q.11 _____ is the radix of Hexadecimal number

Q.12 The complimentary function is represented by _____ gate.

(2) 120955/30955/105855

- Q.13 Demultiplexer is the reverse of _____.
- Q.14 According to Boolean Algebra $A(A+B)=$ _____
- Q.15 SR flip flop has active input as _____
- Q.16 A half adder includes a NAND gate with _____ gate.
- Q.17 The commonly used D/A converter is a _____ network
- Q.18 The program counter in the 8085 microprocessor is of _____ bit
- Q.19 The power consumption of LCD is _____ than LED.
- Q.20 TTL stands for _____

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Convert C5E2F826 to binary.
- Q.22 What is difference between analog & digital signals?
- Q.23 Explain with the help of truth table, the working of OR and AND gates.
- Q.24 State and prove De-morgan's Theorems.
- Q.25 What is the difference between combinational and sequential circuit.
- Q.26 What is J-K flip-flop? What are its advantages over S-R flip flops?
- Q.27 Why are A/D and D/A converters necessary?
- Q.28 What are various registers of 8085 ? Discuss their function
- Q.29 Draw the PIN diagrams of 8085

(3) 120955/30955/105855

- Q.30 Write a short note on Counters?
- Q.31 Write an assembly language program to add two numbers and store your result in memory location 2003H ?
- Q.32 What are universal gates ? Why these are called as universal ?
- Q.33 Discuss in brief different types of semiconductor memories ?
- Q.34 Explain the difference between static and dynamics memories
- Q.35 Define the term bit, byte and word.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Draw block diagram of 8085 microprocessor ? what are different addressing modes of 8085 ?
- Q.37 Simplify the function using K-map
 $Y=(A,B,C,D) = \sum m(1,3,7,11,13) + D(0,2,5)$
- Q.38 Write short note on :
 (i) D/A converters
 (ii) A/D converters

(1120)

(4) 120955/30955/105855