

- Q.29 Differentiate between band pass filter and band elimination filter?
- Q.30 Define Z and Y parameters of a two part networks?
- Q.31 How impedance matching is done using STUBS? Briefly describe the methods used.
- Q.32 Deduce a relationship between VSWR and reflection coefficient K.
- Q.33 What are the advantages of m-derived filter?
- Q.34 Explain how a minimum loss attenuator is designed?
- Q.35 What do you mean by loading? How is it done?

SECTION-D

- Note:** Long Answer type question. Attempt any two questions out of three questions. (2x10=20)
- Q.36 How a transmission line is represented by a T-type circuit? Derive the expression for its characteristic's impedance.
- Q.37 Draw and explain the working of butter worth's first order low Pass Filter and derive equations for it.
- Q.38 Write a short note on any two of the following:
- Applications of transmission lines
 - Bridge T attenuator
 - Constant K high pass filter

No. of Printed Pages : 4
Roll No.....

171041/121041/31041

4th Sem / Eltx. Engg. Power Eltx Engg. Subject : Network Filters & Transmission Lines

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory. (10x1=10)

- Q.1 For a symmetrical network:
- $h_{11} h_{22} - h_{12} h_{21} = 1$
 - $h_{11} h_{22} - h_{12} h_{21} = 0$
 - $h_{12} = h_{21}$
 - $h_{11} = h_{22}$
- Q.2 A two port is reciprocal if and only if:
- $Z_{11} = Z_{22}$
 - $Y_{12} = -Y_{21}$
 - $H_{12} = H_{21}$
 - $AD - BC = -1$
- Q.3 Neper is equal to _____
- 115.1 x attenuation is dB
 - 11.51 x attenuation is dB
 - 1.151 x attenuation in dB
 - 0.1151 x attenuation in dB
- Q.4 An attenuator have applications in _____
- AC & DC circuits
 - AC circuit only
 - DC circuit only
 - Low frequency applications only

- Q.5 An m-derived filter with $m=1$ is same as _____
 a) equalizer b) attenuator
 c) butterworth filter d) prototype filter
- Q.6 For a prototype LPF, the phase constant β in the attenuation band is given by _____
 A) π b) 0
 C) $\pi/2$ d) $\pi/4$
- Q.7 A filter having two stop bands and separated by a small pass band is called _____
 a) LPF b) BPF
 c) BSF d) HPF
- Q.8 If $K=0$, then VSWR will be _____
 a) 0 b) 1
 c) 2 d) ∞
- Q.9 Phase constant β in HF line is _____
 A) $\omega L/C$ b) $\omega/\omega_c L$
 C) $\omega/\omega_c L$ d) $\omega_c L$
- Q.10 Transmission line will be distortion less is _____
 a) $LC=GR$ b) $LG=1/CR$
 c) $LG=CR$ d) $LR=GC$

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Draw a Unilateral network?

- Q.12 What is h-parameters?
- Q.13 What do you mean image impedance?
- Q.14 What do you mean by active filters?
- Q.15 What is asymmetrical network?
- Q.16 Name any two types of distortion in transmission lines.
- Q.17 Draw the diagram of prototype of low pass T filter.
- Q.18 What is the formula for cut-off frequency of BSF?
- Q.19 What is the full form of VSWR?
- Q.20 Define the term dielectric loss.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 What are active and passive filters?
- Q.22 How you can distinguish between symmetrical and asymmetrical networks?
- Q.23 What do you mean by transmission lines? What are its various types?
- Q.24 Derive an expression for open circuit impedance of half section.
- Q.25 Explain different electrical parameters of a symmetrical networks.
- Q.26 What is an attenuator? Name its various types.
- Q.27 Write a short note on attenuation constant of a transmission line.
- Q.28 Explain the design of symmetrical π network.