

No. of Printed Pages : 4  
Roll No. ....

220824

**2nd Sem./ Computer, Computer  
( For Speech and Hearing Impaired)  
Subject : Analog Electronics**

Time : 3 Hrs.

M.M. : 60

**SECTION-A**

**Note:** Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 The number of diodes required in half wave rectifier. (CO3)

- a) 4                                      b) 2
- c) 1                                      d) None

Q.2 Diode normally works in (CO1)

- a) Forward Bias                      b) Reverse Bias
- c) Both                                      d) None

Q.3 Majority carriers in P-type semiconductors is (CO1)

- a) Holes                                      b) Electrons
- c) Both                                      d) None

Q.4 The temperature Coefficient of Semiconductor is (CO1)

- a) Positive                                      b) Negative
- c) Zero                                      d) None of the above

Q.5 BJT Stands for (CO2)

- a) Bi-junction transfer
- b) Blue Junction Transfer
- c) Bipolar Junction Transistor
- d) Base junction Transistor

Q.6 An oscillator converts \_\_\_\_\_ (CO4)

- a) A.C Power to D.C Power
- b) D.C. Power to A.C Power
- c) Mechanical Power into A.C Power
- d) None of the above

**SECTION-B**

**Note:** Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 Expand MOSFET. (CO2)

Q.8 Define Knee Voltage. (CO1)

Q.9 What is Op-Amp? (CO5)

- Q.10 What is Filter? (CO3)
- Q.11 Define Doping? (CO1)
- Q.12 FET stands for \_\_\_\_\_. (CO4)

- Q.22 Write short note on : (CO2)
- a) FET
- b) MOSFET

### SECTION-C

**Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Explain mechanism of current in PNP transistor. (CO2)
- Q.14 Draw and explain a potential divider circuit. (CO2)
- Q.15 Difference between intrinsic and extrinsic semiconductor (CO1)
- Q.16 Explain working of inverting amplifier? (CO5)
- Q.17 Explain working of a RC Phase shift oscillator. (CO4)
- Q.18 Discuss Working of 7805 Regulator (CO3)
- Q.19 Write short note on Pi Filter. (CO3)
- Q.20 What is need of a Multistage amplifier. (CO4)
- Q.21 Explain Formation of Potential Barrier of P-N Junction. (CO1)

(3) 220824

### SECTION-D

**Note:** Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Differentiate conductors, semiconductors and insulators on the basis of their energy level diagram. (CO1)
- Q.24 Explain the working of bridge rectifier. (CO3)
- Q.25 Write short note on : (CO5)
- a) Op-AMP
- b) CRT

(5540) (4) 220824