

- Q.32 Explain different types of semiconductor memories
 Q.33 Explain the Flag register of 8085
 Q.34 Explain the addressing modes of 8085
 Q.35 Explain briefly the 8257 DMA controller

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 With a neat sketch explain the working of R-2R D/A converter
 Q.37 Minimize using K-map and implement using NAND gates

$$f(A,B,C,D) = \sum (0,2,7,8,13,15) + \sum d(4,5,10,14)$$

- Q.38 Draw the pin diagram of 8085 and explain the role of each pin

No. of Printed Pages : 4
 Roll No.

120955/030955/105855

5th Sem / Elect, GE, Power Station Engg. Subject:- Digital Electronics and Microprocessors

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The gate whose output is 1 when the two of its inputs are 1 and 0 is
 a) AND b) OR
 c) NOR d) All of the above
- Q.2 A half adder can be constructed using a AND gate and _____ gate
 a) NOR b) OR
 c) Ex-OR d) NAND
- Q.3 Race around condition is exhibited by _____ Flip flop
 a) RS b) JK
 c) T d) D
- Q.4 Combining of 4 elements in a k-map results in reduction of _____ variables from o/p
 a) 1 b) 2
 c) 3 d) 4

- Q.5 Clock frequency of 8085 is
a) 1 MHz b) 2 MHz
c) 3 MHz d) 4 MHz

- Q.6 A Not gate has _____ inputs
a) 1 b) 2
c) 3 d) 4

- Q.7 Binary equivalent of 15 is
a) 1101 b) 1011
c) 1110 d) 1111

- Q.8 2's complement representation of -8 is
a) 00001000 b) 00000111
c) 11110111 d) 11111000

- Q.9 Nonmaskable interrupt of 8085 is
a) INTR b) RST 6.5
c) RST 5.5 d) TRAP

- Q.10 Interrupt with the lowest priority is
a) INTR b) RST 6.5
c) RST 5.5 d) TRAP

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Half adder has 3 inputs (True/False)
Q.12 Ex-Or gate is a universal gate (True/False)

- Q.13 Draw the symbol of EX-Nor Gate

- Q.14 $(1101)_{16} = (?)_{10}$

- Q.15 $A+1 = A$ (True/False)

- Q.16 $A + \bar{A} = 0$ (True/False)

- Q.17 8:1 Mux has _____ Select lines

- Q.18 Define wait state

- Q.19 8085 is _____ bit microprocessor

- Q.20 Full form of ALE is _____

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 $(235)_8 = (?)_{10} = (?)_{16}$

- Q.22 Explain demorgan's second theorem

- Q.23 Explain the working of 4:1 MUX

- Q.24 Explain the working of a Full Adder

- Q.25 Differentiate between encoder and decoder

- Q.26 Minimize using Boolean algebra $F(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$

- Q.27 Draw the truth table of JK Flip flop

- Q.28 Differentiate between SOP and POS

- Q.29 Explain 1:4 DEMUX

- Q.30 Explain the use of NAND gate as universal gate

- Q.31 Explain successive approximation A/D converter