

- Q.30 What is difference between AC and DC? (CO-6)
- Q.31 Explain the vector representation of alternating quantities. (CO-6)
- Q.32 Explain the concept of susceptance and admittance. (CO-7)
- Q.33 Explain active and reactive components of current and its significance. (CO-7)
- Q.34 Write advantages of 3 phase over single phase. (CO-8)
- Q.35 Explain power in 3 phase circuits. (CO-8)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain working principle and applications of Nickle Cadmium Cell. (CO-3)
- Q.37 Explain “energy stored in a magnetic field.” (CO-5)
- Q.38 Give expression of impedance, phase angle, power factor of single-phase ac supply delivering to RLC series circuit. (CO-7)

Note : Course Outcome (CO) mentioned in the question paper is for official purpose only.

No. of Printed Pages : 4

120926

Roll No.

Branch : 2nd Sem Elect/Elect. & Eltx Engg/Fire Tech & Safety
Subject : Fundamental of electrical engineering

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The shape of AC is (CO-1)
- Straight horizontal Line
 - Square wave
 - Sine wave
 - Triangular wave
- Q.2 In India, frequency of DC supply is (CO-1)
- 0
 - 50
 - 100
 - 230
- Q.3 Equivalent resistance of two resistance 10 ohm each in series in (CO-2)
- 0
 - 5
 - 10
 - 20
- Q.4 In a primary cell, chemical reactions taking place are (CO-3)
- Reversible
 - Irreversible
 - Both
 - None of above
- Q.5 Average emf of lead acid cell is (CO-3)
- 1.0 V
 - 1.2 V

- c) 1.8 V d) 2.0 V
- Q.6 The Hysteresis loss is caused by (CO-4)
 a) Structural non-homogeneity
 b) Work required for the magnetising the material
 c) Potential work function
 d) None of above.
- Q.7 The property of coil by which a counter e.m.f. is induced in it when the current through the coil changes is known as (CO-5)
 a) Self inductance b) Mutual inductance
 c) Conductance d) Admittance
- Q.8 The power factor at resonance in R-L-C- parallel circuit is (CO-6)
 a) 0 b) 0.8 lagging
 c) 0.8 leading d) Unity
- Q.9 In a three-phase system, the voltages are separated by (CO-8)
 a) 45° b) 90°
 c) 120° d) 180°
- Q.10 Eddy current will depend upon (CO-5)
 a) Frequency b) Flux density
 c) Thickness d) All of above

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Define Ac. (CO-1)
 Q.12 Define Charge. (CO-1)

(2)

120926

- Q.13 Define e.m.f. (CO-2)
 Q.14 Define Cell. (CO-3)
 Q.15 Define hysteresis loop. (CO-4)
 Q.16 Define mutual induction. (CO-5)
 Q.17 Define rms value (CO-6)
 Q.18 Define phase difference. (CO-6)
 Q.19 Define conductance (CO-7)
 Q.20 What is star connection (CO-8)

SECTION-C

Note: Short answer type questions. Attempt any Twelve questions out of fifteen questions. (12x5=60)

- Q.21 What are the advantages of electrical energy?(CO-1)
 Q.22 Explain Ohm's Law. Explain resistance in series. (CO-2)
 Q.23 Explain Kirchhoff's first law. (CO-2)
 Q.24 How care and maintenance of lead acid battery done? (CO-3)
 Q.25 What are charging methods used for lead acid accumulator. (CO-3)
 Q.26 Write a short note on "Magnetic field across straight current carrying conductor." (CO-4)
 Q.27 What is force between two parallel current carrying conductors? (CO-4)
 Q.28 Explain Lenz's law. (CO-5)
 Q.29 Explain the concept of eddy currents and eddy current losses. (CO-5)

(3)

120926