

- Q.28 Define interrupt and types of interrupt used in 8085. (CO9)
- Q.29 Explain octal to Binary encoder. (CO4)
- Q.30 Explain NAND Gate with Truth Table. (CO2)
- Q.31 Define Flip-Flop and explain S-R Flip-Flop. (CO5)
- Q.32 Differentiate between combinational and sequential circuit. (CO4)
- Q.33 Explain the following instructions. (CO9)
- a) POP
 - b) MOV
- Q.34 Define De Morgan's Theorems. (CO3)
- Q.35 Simplify the Expression $(A+B)(A+C)$

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. $(2 \times 10 = 20)$

- Q.36 Explain universal gate. Realize NOT, AND, OR using NAND Gate. (CO2)
- Q.37 Minimise the following expression by using K-map and realize the result by using NAND gates $Y = \sum m(0,1,4,5,12,13,8,9,2,6,14)$. (CO3)
- Q.38 Explain the followings:
- a) Successive approximation A/D converter. (CO7)
 - b) Application of Flip-Flops. (CO5)

No. of Printed Pages : 4 120955/030955/105855
Roll No.

5th Sem / Elect, GE, Power Station Engg.
Subject:- Digital Electronics and Microprocessors

Time : 3Hrs. M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory $(10 \times 1 = 10)$

- Q.1 A NAND gate is equivalent to an AND gate followed by _____ gate. (CO1)
- a) XOR
 - b) NOT
 - c) OR
 - d) NOR
- Q.2 The number of select line for 4:1 MUX are _____. (CO4)
- a) 6
 - b) 4
 - c) 2
 - d) 3
- Q.3 $A \cdot \bar{A} =$ (CO3)
- a) 1
 - b) 0
 - c) A
 - d) \bar{A}
- Q.4 A half adder can add _____ number of bits. (CO4)
- a) 1
 - b) 3
 - c) 2
 - d) 4

- Q.5 Radix of octal number system is _____. (CO1)
 a) 6 b) 8
 c) 16 d) 2
- Q.6 How many bits make a Nibble? (CO1)
 a) 4 Bits b) 8 Bits
 c) 16 Bits d) 2 Bits
- Q.7 The 2's complement of 0110101 binary is (CO1)
 a) 110001 b) 001001
 c) 1001011 d) 111001
- Q.8 The basic storage element is a digital system is _____. (CO7)
 a) Flip-Flop b) Counter
 c) MUX d) Encoder
- Q.9 How many bit program counter is available in 8085? (CO8)
 a) 8 Bit b) 16 Bit
 c) 32 Bit d) Both a and b
- Q.10 The highest priority interrupt in 8085 is _____. (CO9)
 a) TRAP b) RST6.5
 c) INTR d) RST7.5

(2) 120955/030955/105855

SECTION-B

- Note:** Objective type questions. All questions are compulsory. (10x1=10)
- Q.11 $1001+1100=$ _____ (CO1)
- Q.12 PIPO stands for _____. (CO6)
- Q.13 Define combinational circuit. (CO4)
- Q.14 Write full form of LCD. (CO8)
- Q.15 Draw the symbol of EX-OR gate. (CO2)
- Q.16 The number of digits in hexadecimal system. (CO1)
- Q.17 Define Minterm. (CO3)
- Q.18 EEPROM stands for _____. (CO8)
- Q.19 Define Encoder. (CO4)
- Q.20 Define ALU. (CO9)

SECTION-C

- Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)
- Q.21 Design and implement a half adder with neat diagram. (CO4)
- Q.22 What are different type of semiconductor memory. (CO8)
- Q.23 Write short note an D/A Converter. (CO7)
- Q.24 Compare 8-bit & 16-bit microprocessor. (CO9)
- Q.25 Differentiate between latch and flip flop. (CO5)
- Q.26 Convert $(8.625)_{10}$ to binary. (CO1)
- Q.27 Write short note on 8:1 MUX. (CO4)

(3) 120955/030955/105855