

No. of Printed Pages : 4

221014/212817

Roll No.

**1st Sem / ECE/ Instrumentation & Control engg.
/ Automation & Robotics / Medical electronics/ ECE
(For Speech and Hearing Impaired)**

**Subject : Fundamentals of Electrical Engineering /
Fundamentals of Electrical Engg**

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 Unit of Power is

- | | |
|----------|----------|
| a) Volt | b) Joule |
| c) Farad | d) Watt |

Q.2 Unit of Current is

- | | |
|-----------|----------|
| a) Ampere | b) Ohm. |
| c) Watt. | d) Volt. |

Q.3 Minimum value of power factor is

- | | |
|-------|-------|
| a) -1 | b) 0 |
| c) -2 | d) -3 |

Q.4 Power consumed by pure capacitor is equal to

- | | |
|-------------|--------|
| a) Infinite | b) 0 |
| c) 1 | d) 200 |

(1)

221014/212817

Q.5 Unit of M.M.F is

- | | |
|-----------|-----------------|
| a) Ampere | b) Ampere Turns |
| c) Volt | d) Watt |

Q.6 At time of series Resonance the value of current is

- | | |
|------------|------------|
| a) Maximum | b) zero |
| c) One | d) Minimum |

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 Power is measured by _____

Q.8 As the length of conductor increases, it's resistance Increases/ Decreases.

Q.9 Unit of Capacitance is _____

Q.10 Phase difference between voltage and current in pure inductor is _____

Q.11 Resistors of 6W and 3W are connected in series their total resistance is equal to _____.

Q.12 Reciprocal of Resistance is _____.

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

Q.13 Define and explain Thevenin theorem.

(2)

221014/212817

- Q.14 Define and explain KCL.
- Q.15 Define and explain Ohm's law.
- Q.16 Define & explain Frequency, Amplitude.
- Q.17 Define & explain R.M.S. value of A.C.
- Q.18 Explain difference between A.C and D.C
- Q.19 Draw and explain Impedance triangle for R-L series circuit.
- Q.20 Explain power factor and its significance.
- Q.21 Explain series and parallel combination of Inductors.
- Q.22 Explain the concept of self Inductance.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Explain Voltage and current source, symbol & Characteristics of ideal and practical sources.
- Q.24 Explain construction, working principle and applications of lead Acid Batteries.
- Q.25 Explain Star to Delta and Delta to Star conversion.