

- Q.26 Explain the concept of Infinite line. CO-3
- Q.27 Prove that for symmetrical T Network $Z_o^2 = Z_{oc} * Z_{sc}$ CO-1
- Q.28 Define Attenuator. Explain its various types. CO-2
- Q.29 Give five application of Transmission Line. CO-4
- Q.30 Give the applications of Filters. CO-3
- Q.31 Derive an expression for characteristic impedance of T network. CO-1
- Q.32 What is distortion? Explain different types of Distortion? CO-3
- Q.33 Explain Secondary Constant of Transmission Line. CO-3
- Q.34 Derive the design equation of Symmetrical T network. CO-2
- Q.35 List five advantages of Active Filter. CO-3

SECTION-D

- Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)
- Q.36 What is Network? Explain the concept of symmetrical and Asymmetrical Network and the parameters associated with them. CO-1
- Q.37 Define Filter. Deduce the relationship between Characteristics Impedance and frequency for low Pass filter. Draw its curve also. CO-3
- Q.38 Define Transmission Line. Explain its various types in elaborated manner. CO-4

No. of Printed Pages : 4

Roll No.

171041/121041/031041

4th Sem / Branch : Eltx, Power Eltx

Subject:- Network Filters and Transmission Lines


Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

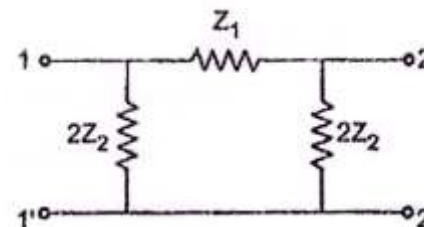- Q.1 How many terminals a two port network has CO-1
- a) 1 b) 2
- c) 3 d) 4
- Q.2 Network shown below is _____ network. CO-1



- a) Symmetrical, T Section
- b) Asymmetrical T Section
- c) Symmetrical, π Section
- d) Asymmetrical, π Section
- Q.3 Attenuation in dB = _____ * attenuation in Neper CO-2
- a) 5.626 b) 8.686
- c) 3.172 d) 9.812

- Q.4 Attenuation in any symmetrical attenuator is given by CO-2
 a) $a=20\log\sqrt{I_1R_1/I_2.R_2}$ b) $a=20\log\sqrt{I_1/I_2}$
 c) $a=20\log I_1/I_2$ d) $a=10\log I_1/I_2$
- Q.5 A filter which allow to pass signal of all frequencies upto particular frequency and stop signal cut off frequency is called CO-3
 a) High Pass Filter b) Low Pass Filter
 c) Band Pass Filter d) Band Stop Filter
- Q.6 For a prototype LPF, characteristic impedance at $f=0$ is given by CO-3
 a) $\sqrt{L/C}$ b) $1/\sqrt{LC}$
 c) \sqrt{LC} d) $\sqrt{C/L}$
- Q.7 An ideal filter should have _____ attenuation in the pass band. CO-3
 a) Zero b) Infinite
 c) R^2 d) Z_0
- Q.8 In a lossless line, characteristic impedance is given by CO-4
 a) $\sqrt{L/C}$ b) $\sqrt{R+j\omega L}$
 c) L/C d) $\sqrt{R+(j\omega L)(G+j\omega C)}$
- Q.9 S is given by CO-4
 a) $1+1/K1/1-1/K1$ b) $1-1/K1/1+1/K1$
 c) $(1-1/K1)(1+1/K1)$ d) $(1+1/K1)e^{(1-1/K1)}$
- Q.10 Primary constants of a line are CO-4
 a) R, L, Z_0 and g b) R, L, G and C
 c) Z_0, g, a and b d) G, C, b and a

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 A network with electrical characteristic : Iterative impedance, Image impedance, Iterative transfer constant, Image transfer constant is called _____ network. CO-1
- Q.12 Define Characteristic Impedance. CO-1
- Q.13 Define Insertion loss. CO-1
- Q.14 Define Attenuation. CO-2
- Q.15 What are characteristics of Attenuators? CO-2
- Q.16 Define Cutoff frequency. CO-3
- Q.17 Draw Prototype lowpass filter. CO-3
- Q.18 Define transmission line. CO-4
- Q.19 Draw Equivalent circuit of transmission line. CO-4
- Q.20 Define Reflection coefficient. CO-4

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain the difference between Asymmetrical and Symmetrical Network. CO-1
- Q.22 Explain the uses of Attenuator. CO-2
- Q.23 What are the limitations of Prototype Filter? CO-3
- Q.24 Explain the difference between Active Filter and Passive Filter. CO-3
- Q.25 Derive the relationship between Reflection coefficient and VSWR. CO-4