

- Q.25 Explain R/2R Ladder Digital to Analog Converter.
- Q.26 Write a short note on PLA.
- Q.27 What is difference between EPROM and EEPROM.
- Q.28 Design a MOD - 10 or Decade Counter using J-K Flip Flop.
- Q.29 Explain in brief about different types of Sequential Circuits.
- Q.30 Write any five differences between Static and Dynamic memories.
- Q.31 Simplify using K-map

$$U = \sum(1,2,3,5,6,7,9,13,14)$$
- Q.32 Draw the logic circuit diagram of IC 74181.
- Q.33 Write a short note on Fuzzy Set.
- Q.34 Describe Membership Function and its properties.
- Q.35 Write a short note on Moore Machine.

SECTION-D

- Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)
- Q.36 What is memory? Explain in brief about the classification of memory.
- Q.37 Simplify the following logic expression by using the Quine Mccluskey method

$$f = \sum(a,b,c,d) \sum m(0,1,2,5,6,7,8,9,10,14)$$
- Q.38 Explain the working of Dual Slope Analog to Digital converter with the help of circuit diagram.

No. of Printed Pages : 4

121044/31044

Roll No.

4th Sem / Eltx, Med Eltx, Power Eltx Subject:- Digital Electronics - II

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The Unipolar logic family uses only
 a) npn Transistor b) pnp Transistor
 c) MOS device d) None of the above
- Q.2 The number of gates in LSI are
 a) 100 to 999 b) 1000 to 9999
 c) Over 10000 d) 12 to 99
- Q.3 Which type of register used in Successive Approximation type A/D Converter is
 a) SISO b) PISO
 c) SIPO d) SAR
- Q.4 RAM stands for
 a) Really old memory
 b) Read only memory
 c) Random access memory
 d) Redundancy only memory

- Q.5 Information in a memory chip is stored in _____ form.
- a) Analog b) Digital
c) Both d) None
- Q.6 How many cells are there in a four variable k-map?
- a) 4 b) 16
c) 8 d) 15
- Q.7 How many variables are reduced when the grouping of eight cells are done?
- a) 1 b) 2
c) 3 d) 4
- Q.8 The class B & C machines are also called
- a) Mealy Machine b) Moore Machine
c) Finite State Machine d) None of the above
- Q.9 IC 74181 have pins
- a) 26 b) 28
c) 14 d) 24
- Q.10 Which one of the following is a membership function.
- a) μ membership function
b) S - membership function
c) Gaussian membership function
d) All of the above

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 _____ is the fastest logic family.
- Q.12 TTL stands for _____.
- Q.13 Write the name of two methods of Digital to Analog converter.
- Q.14 CCD stands for _____.
- Q.15 EPROM is _____ (Volatile/Non-Volatile) memory.
- Q.16 The min terms are represented by _____ in a k-map.
- Q.17 The number of Flip Flops required for a decade counter is _____.
- Q.18 The Speed of an Asynchronous counter is _____ than that of synchronous counter.
- Q.19 IC 74181 is used for _____.
- Q.20 MOM stands for _____.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Define Fan in and Fan out for a logic family.
- Q.22 Write a short note on MOS.
- Q.23 How digital ICs are classified on the basis of packing density?
- Q.24 Explain any five characteristics of Digital to Analog Converter.