

- Q.27 What are the various advantages of electrical energy? (CO-1)
- Q.28 Difference between a.c. and d.c. (CO-1)
- Q.29 How much energy is stored in the inductor? Discuss in detail. (CO-4)
- Q.30 Define active and reactive power. (CO-3)
- Q.31 Write significance of power factor. (CO-6)
- Q.32 Explain star-delta conversion with formula. (CO-1)
- Q.33 Explain superposition theorem. (CO-2)
- Q.34 Explain the series and parallel combination of inductor with circuit diagram. (CO-4)
- Q.35 Write a short note of Fleming's left hand rule. (CO-5)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain the construction, principle and working of lead acid cells. (CO-5)
- Q.37 Explain following: (CO-3)
- a) Average value b) RMS value
- c) Frequency d) Instantaneous value
- Q.38 Explain Faraday's law of electromagnetic induction. What is self inductance and mutual inductance? (CO-4)

(**Note:** Course outcome/CO is for office use only)

No. of Printed Pages : 4

Roll No.

202425/171027/

120828/030828

**2nd Sem / Branch : Comp, ECE, IT, I & control,
Med. Eltx, Eltx & Instr., Power Eltx, EEE
Subject:- Basic Electrical Engineering**

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 Energy stored in a magnetic field is measured in (CO-4)
- a) kWh b) Coulombs
- c) joules d) Watts
- Q.2 Direction of induced, emf is found by (CO-4)
- a) Fleming's Left hand rule
- b) Fleming's Right hand rule
- c) b and c both
- d) lenz's law
- Q.3 The form factor will be equals to (CO-3)
- a) 1.0 b) 1.1
- c) 1.187 d) 1.100
- Q.4 Which of the following is the unit of inductance? (CO-3)
- a) Ohm b) Henery
- c) Faraday d) none

- Q.5 Thevenin's equivalent circuit consists of (CO-2)
- Series combination of R_{th} , V_{th} & R load
 - V_{th} and R_{th} in series
 - V_{th} and R_{th} in parallel
 - None of these
- Q.6 The specific gravity of acid is checked with the help of which equipment (CO-5)
- Hydrometer
 - Hygrometer
 - Lactometer
 - Cell tester
- Q.7 Which of the following has a negative temperature coefficient? (CO-4)
- Electrolytes
 - brass
 - silver
 - mercury
- Q.8 Kilowatt-hour(kWh) is a unit of (CO-1)
- Current
 - Power
 - Energy
 - Resistance
- Q.9 Unit of magnetomotive force is (CO-4)
- Weber
 - Tesla
 - Amp-turns
 - Reluctance
- Q.10 A tuned circuit uses (CO-5)
- R-L
 - R-C
 - L-C
 - Both a and b

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Unit of current is _____ (CO-1)
- Q.12 Frequency of D.C. is _____ (CO-1)
- Q.13 The unit of conductivity is _____ (CO-3)
- Q.14 Define battery. (CO-5)
- Q.15 Define Primary cells. (CO-5)
- Q.16 In a pure inductor the voltage _____ the current by 90. (CO-3)
- Q.17 Resistance is inversely proportional to ____ (CO-1)
- Q.18 What are active components? (CO-1)
- Q.19 In a circuit voltage is measured by _____ (CO-2)
- Q.20 The device which converts AC into DC is called. _____ (CO-1)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Define flux and reluctance. (CO-4)
- Q.22 Explain ohm's law. (CO-2)
- Q.23 Explain KCL and KVL with their symbols. (CO-2)
- Q.24 What is resonance? Explain parallel resonance in detail. (CO-3)
- Q.25 Explain RL series circuit with circuit diagram. (CO-3)
- Q.26 Give an idea about solar panels and write their applications. (CO-5)