

SECTION-B

Note: Short answer type questions. Attempt any six questions out of eight questions. (6x5=30)

- Q.11 What are the advantages of digital system over analog system?
- Q.12 State and explain Demorgan's law
- Q.13 Implement OR & And gate using NAND gates only.
- Q.14 Explain in brief about the Truth Table, Boolean expression and logic diagram of Full Adder.
- Q.15 Explain the operation of SR Flip Flop with diagram.
- Q.16 Explain 7 Segments display in brief.
- Q.17 Explain PIPO Shift Register with diagram.
- Q.18 Differentiate between Static and Dynamic memories.

SECTION-C

Note: Long answer type questions. Attempt any one question out of two questions. (1x10=10)

- Q.19 Define Multiplexer. Design a 32:1 Mux by using 16:1 Mux and 2:1 Mux.
- Q.20 Explain the working of 4 bit Asynchronous Counter with the help of Truth Table and Pulse diagram.

No. of Printed Pages : 2
Roll No.

188543

2nd Sem, Level 4 / DVOC (Medical Imaging Tech., SD)
Subject : Digital Electronics

Time : 2 Hrs.

M.M. : 50

SECTION-A

Note: Very short questions. Attempt all ten questions. (10x1=10)

- Q.1 Define Analog signal.
- Q.2 In a Boolean algebra $X + 1 =$
- Q.3 Which gate can be used as an inverter?
- Q.4 Draw the symbol of NOR gate?
- Q.5 Define Combinational circuit.
- Q.6 Write the truth table of Half Adder
- Q.7 How many output data lines are there in a 32:1 multiplexer?
- Q.8 Define Flip Flop
- Q.9 How many Flip Flops are required to build up MOD 6 counter.
- Q.10 Expand LCD