

No. of Printed Pages : 4

180962/170962

Roll No.....

6th Sem,

Branch : Electrical Engg.

Sub. : Industrial Electronics & Control of drives (IECD)

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note : Multiple choice questions. All questions are compulsory. (10x1=10)

- Q.1 An SCR is a _____ switch. (CO-1)
a) Unidirectional b) Bidirectional
c) Three directional d) Four directional
- Q.2 Inverter converts (CO-5)
a) AC to DC b) DC to AC
c) DC to DC d) AC to AC
- Q.3 A cyclo-converter is a _____ (CO-7)
a) One stage power converter
b) One stage voltage converter
c) One stage frequency converter
d) None of the above
- Q.4 SCRs are connected in parallel to fulfill the _____ demand. (CO-1)
a) High voltage b) High current
c) Size d) Efficiency
- Q.5 If the firing angle in an SCR rectifier is decreased, the output is (CO-4)

(1)

180962/170962

- a) Increased b) Decreased
c) Maximum d) Remain unaffected

- Q.6 The most suitable method to turn on the SCR device is (CO-1)
a) Gate Triggering Method
b) Forward Voltage Triggering Method
c) Temperature Triggering Method
d) dv/dt triggering Method
- Q.7 Which method is used to control the speed of DC shunt motor above normal speed? (CO-3)
a) Armature voltage control method
b) Flux control method
c) Both option (1) & (2)
d) None of the above
- Q.8 Static UPS requires (CO-5)
a) Only Rectifier
b) Only Inverter
c) Both Rectifier & Inverter
d) None of the above
- Q.9 A DIAC is turned on by (CO-1)
a) Breakover voltage b) Gate Current
c) Gate Voltage d) None of the above
- Q.10 A DC Chopper controls the average voltage across the DC motor by controlling. (CO-3)
a) Input voltage b) Field current
c) Line current d) Duration of T_{on} & T_{off}

(2)

180962/170962

Section B

Note: Objective types Questions. All Questions are compulsory. (10x1=10)

- Q.11 List any one application of TRIAC. (CO-2)
- Q.12 Draw symbol of DIAC. (CO-1)
- Q.13 Define Electric drive. (CO-7)
- Q.14 Write the purpose of freewheeling diode. (CO-4)
- Q.15 Define commutation. (CO-1)
- Q.16 Define trickle charging. (CO-6)
- Q.17 Write two applications of cyclo-converter. (CO-7)
- Q.18 In which quadrant class D chopper operates (CO-3)
- Q.19 Name any one device that belongs to Thyristor family. (CO-1)
- Q.20 Write full form of SMPS. (CO-6)

Section-C

Note: Short answer type Questions. Attempt any twelve Questions out of fifteen Questions. (12x5=60)

- Q.21 Draw the VI Characteristics of UJT and explain it working. (CO-1)
- Q.22 Explain two transistor analogy of an SCR. (CO-1)
- Q.23 Explain the circuit diagram for single phase, half controlled full wave rectifier. (CO-4)
- Q.24 Explain the working of step down chopper with the help of circuit diagram. (CO-3)
- Q.25 Define cycloconverter. Describe basic principle of its operation. (CO-7)
- Q.26 Explain fan speed control circuit using Triac. (CO-2)

- Q.27 Describe the concept of protection of thyristor. (CO-1)
- Q.28 Describe briefly the slip control of AC drive. (CO-7)
- Q.29 Draw and explain the block diagram of dual converter. (CO-7)
- Q.30 Define UPS and explain the working of an line UPS. (CO-5)
- Q.31 Explain the importance of heat sink and criterion of selection for thyristor. (CO-1)
- Q.32 List five instructions for maintenance and care of Lead Acid batteries. (CO-6)
- Q.33 List five advantages of SMPS over conventional power supply. (CO-7)
- Q.34 Write a short note on CVT. (CO-7)
- Q.35 Define commutation. Explain natural commutation. (CO-1)

Section-D

Note: Long answer Questions. Attempt any two Questions out of three Questions. (2x10=20)

- Q.36 Draw VI characteristics of SCR. Explain the construction and working of SCR. (CO-1)
- Q.37 Explain the working of a current source series inverter with the help of circuit diagram. Write the drawbacks of series inverter. (CO-7)
- Q.38 Explain the speed control method for DC motor using dual converter with proper circuit diagram. (CO-3)