

- 202451

Subject:- Power Electronics

M.M. : 100

- ## SECTION-A

a) 12 b) 3
c) 4 d) 1

- [illegible]

- a) 12 b) 3
c) 4 d) 5

- a) P-N-P b) P-N-P-N
c) N-P-N d) P-N

- a) Equal b) more
c) less d) zero

- Q.6 Inverter converts (CO3)
 a) AC into DC b) DC into AC
 c) AC into AC d) None
- Q.7 Rectifier converts (CO2)
 a) AC into DC b) DC into AC
 c) AC into AC d) None
- Q.8 Which is used to design Relaxation oscillator? (CO1)
 a) SCR b) DIAC
 c) UJT d) None
- Q.9 UPS has (CO5)
 a) Communication link
 b) Battery
 c) Control circuit
 d) All of above
- Q.10 Cycloconverter is used to change (CO3)
 a) Voltage b) Current
 c) Frequency d) Power

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Expand SCR. (CO1)
- Q.12 Draw the symbol of DIAC. (CO1)
- Q.13 Define latching current. (CO1)
- Q.14 Define commutation. (CO1)

(2)

202451

- Q.15 UPS stands for _____. (CO5)
- Q.16 Draw the symbol of UJT. (CO1)
- Q.17 Define controlled Rectifier. (CO2)
- Q.18 Define Dual Converter (CO3)
- Q.19 Define Drive. (CO4)
- Q.20 SMPS stands for _____. (CO5)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain two transistor analogy of SCR. (CO1)
- Q.22 Explain the need of Heat sink. (CO1)
- Q.23 Draw the characteristics of DIAC. (CO1)
- Q.24 Explain working of TRIAC in brief. (CO1)
- Q.25 Explain speed control of universal motor. (CO1)
- Q.26 Explain working of Half wave controlled rectifier. (CO2)
- Q.27 Draw the circuit Single Phase Full Wave controlled rectifier. (CO2)
- Q.28 Explain the concept of SMPS. (CO5)
- Q.29 Explain working of smart UPS. (CO5)
- Q.30 Explain Half wave DC Drive. (CO4)
- Q.31 Explain working V-F-Drive. (CO4)
- Q.32 Explain working of class A chopper. (CO3)
- Q.33 Explain working of series inverter. (CO3)

(3)

202451