

- Q.7 16:1 Multiplexer has ____ select lines. (CO-7)
 a) 1 b) 2
 c) 4 d) 16
- Q.8 MOD 10 counter requires ____ number of flip flops. (CO-8)
 a) 2 b) 4
 c) 8 d) 10
- Q.9 AND Gate is universal gate. (CO-4)
 a) True b) False
 c) d)
- Q.10 $A + AB =$ ____ (CO-4)
 a) 0 b) 1
 c) A d) B

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Write any two advantages of digitization. (CO-1)
- Q.12 Expand EBCDIC. (CO-2)
- Q.13 Draw symbol of NOR gate. (CO-4)
- Q.14 Define parity. (CO-2)
- Q.15 In Hexadecimal system, how number 14 is represented? (CO-2)
- Q.16 Draw 7 segment display. (CO-7)
- Q.17 Define Latch. (CO-8)
- Q.18 Name any one flip flop IC. (CO-8)

- Q.19 Expand LCD (CO-7)
- Q.20 Define tri state buffer. (CO-8)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Compare TTL & CMOS logic families. (CO-4)
- Q.22 State & Explain Demorgan's theorem. (CO-4)
- Q.23 Draw & Explain EX-OR gate. (CO-4)
- Q.24 Convert $(10101101)_2$ into gray code. (CO-2)
- Q.25 Explain in brief the working of half adder. (CO-7)
- Q.26 Draw the schematic of 1:8 demultiplexer; explain using truth table. (CO-7)
- Q.27 Explain in brief the working of 8:3 encoder. (CO-7)
- Q.28 Draw the schematic & truth table of D flip flop. (CO-8)
- Q.29 Differentiate between asynchronous & synchronous counters. (CO-8)
- Q.30 With the help of diagram, explain SIPO shift register. (CO-8)
- Q.31 What is universal shift register? (CO-8)
- Q.32 Explain in brief the characteristics of D/A converters. (CO-8)
- Q.33 Compare in brief the Mealy & Moore models. (CO-8)
- Q.34 Draw & explain R-2R D/A converter. (CO-8)
- Q.35 Explain the concept of minimal cover table. (CO-8)