

No. of Printed Pages : 4
Roll No.

180962/170962

6th Sem / Branch : Electrical
Sub. : Industrial Electronic & Control of Drives (IECD)

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory
(10x1=10)

- Q.1 The SCR is turned off when the anode current falls below (CO1)
- a) Break over voltage
 - b) Forward current rating
 - c) Latching current
 - d) Holding current
- Q.2 A UJT has _____. (CO1)
- a) One pn junction
 - b) Two pn junction
 - c) Three pn junction
 - d) None of the above
- Q.3 Which device can be used in a chopper circuit? (CO3)
- a) BJT
 - b) MOSFET
 - c) GTO
 - d) All of the above
- Q.4 In the SCR structure the gate terminal is located (CO1)
- a) Near the anode terminal
 - b) Near the cathode terminal
 - c) In between the anode & cathode terminal
 - d) None of the above

(1)

180962/170962

- Q.5 The single phase bridge type cycloconverter uses _____ number of SCRs. (CO7)
- a) Four
 - b) Eight
 - c) Six
 - d) None of the above
- Q.6 The load voltage of a chopper can be controlled by varying the (CO3)
- a) Duty cycle
 - b) Firing angle
 - c) Reactor position
 - d) Extinction angle
- Q.7 Which method is used to control the speed of DC shunt motor above normal speed? (CO3)
- a) Armature voltage control method
 - b) Flux control method
 - c) Both option 1 & 2
 - d) None of the above
- Q.8 SMPS is used of (CO6)
- a) Obtaining controlled ac power supply
 - b) Obtaining controlled dc power supply
 - c) Storage of dc power
 - d) Switch from one source to another
- Q.9 If the firing angle in an SCR rectifier is decreased, the output is (CO4)
- a) Increased
 - b) Decreased
 - c) Maximum
 - d) Remain unaffected
- Q.10 A cyclo-converter is a _____. (CO7)
- a) One stage power converter
 - b) One stage voltage converter
 - c) One stage frequency converter
 - d) None of the above

(2)

180962/170962

SECTION-B

Note: Objective type questions. All questions are compulsory.
(10x1=10)

- Q.11 Define duty cycle. (CO3)
- Q.12 Draw symbol of SCR. (CO1)
- Q.13 Which material is used for making heat sinks. (CO1)
- Q.14 Define inverter. (CO5)
- Q.15 Define Latching current. (CO1)
- Q.16 Write full form of CVT. (CO6)
- Q.17 Which method is used to control the speed of DC shunt motor above normal speed? (CO3)
- Q.18 Define Commutation. (CO1)
- Q.19 List any one application of DIAC. (CO2)
- Q.20 Define UJT. (CO1)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain working of UJT as an Relaxation oscillator. (CO1)
- Q.22 Draw the VI characteristics of DIAC and explain its working.
- Q.23 List five advantages of AC drive over DC Drive. (CO7)
- Q.24 Describe the working of single phase Half controlled half wave rectifier with resistive load. (CO4)
- Q.25 Explain the working principle of series inverter with the help of circuit diagram. (CO5)

(3) 180962/170962

- Q.26 Explain the different methods of triggering of an SCR. (CO1)

- Q.27 Define UPS and explain the working of on line UPS. (CO5)
- Q.28 Explain the series operation of thyristor. (CO1)
- Q.29 Differentiate between Latching current and holding current.
- Q.30 Explain the working of step up chopper with the help of circuit diagram. (CO3)
- Q.31 Explain the working principle of dual converter. (CO7)
- Q.32 List five applications of dual converters. (CO7)
- Q.33 Write a short note on Maintenance of storage devices. (CO6)
- Q.34 Write any five difference between on line ups and off lines UPS. (CO5)
- Q.35 Explain illumination control circuit using TRIAC. (CO2)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Draw VI characteristics of TRIAC. Explain the construction and working of TRIAC. (CO1)
- Q.37 Explain the working of three phase bridge inverter with the help of circuit diagram. (CO5)
- Q.38 Explain the working principle of single phase to single phase cyclo-converter. Also write advantages and disadvantages of cyclo-converter. (CO7)

(4280) (4) 180962/170962