

- Q.28 Give the working principle and V-I characteristics of DIAC. (CO1)
- Q.29 Explain the operation of Dual Converter in Circulating mode with Diagram. (CO3)
- Q.30 What is dynamic and static equalizing circuit? Why these are used in the circuit? (CO3)
- Q.31 Define (CO4)
- Surges
  - Power failure
  - Harmonic distortion
  - Frequency variation
  - Sag
- Q.32 Give the block diagram of UPS and explain its basic parts. (CO5)
- Q.33 Explain Regenerative braking mode with diagram. (CO5)
- Q.34 Give principle of operation of HVDC Transmission. (CO5)
- Q.35 Write merits and demerits of Series Inverter. (CO3)

#### SECTION-D

- Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)
- Q.36 Define construction of SCR with diagram. explain working principle and modes of operation of SCR. (CO1)
- Q.37 Explain the working and diagram of
- Single phase half wave controlled rectifier with resistive load.
  - Single phase half wave controlled rectifier with R-L load with load freewheeling diode. (Co2)
- Q.38 What is a cycloconverter? Explain single phase step up converter. (CO3)

(20) (4) 202451

No. of Printed Pages : 4  
Roll No. ....

202451

#### 5th Sem / Branch : Mechatronics Sub.: Power Electronics

Time : 3Hrs.

M.M. : 100

#### SECTION-A

**Note:** Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The Derating Factor (DRF) is \_\_\_\_\_ given string efficiency = 95% (CO1)
- 0.5
  - 0.05
  - 0.95
  - 0.55
- Q.2 A TRIAC is equivalent to (CO1)
- Two SCRs connected in parallel
  - Two SCRs connected in anti-parallel
  - One diode and one SCR connected in parallel
  - One diode & one SCR connected in anto-parallel
- Q.3 Field control methods is used in D.C. motors to get (CO4)
- Speed above normal speed
  - Speed below normal speed
  - Both A & B
  - None of th above
- Q.4 A step down chopper can give an output voltage (CO3)
- Higher than input voltage
  - Lower than input voltage
  - Both higher and lower than input voltage
  - All of the above

(1) 202451

- Q.5 The duty cycle of a chopper is given by (CO3)  
 a)  $\frac{T_{on}}{T_{off}}$  b)  $\frac{T_{off}}{T_{on}}$   
 c)  $\frac{T_{on}}{T_{on}+T_{off}}$  d)  $\frac{T_{on}}{T_{on}+T_{off}}$
- Q.6 Under voltage for an extended period of time causing equipment to malfunction is known as (CO5)  
 a) Sag b) Surge  
 c) Brownout d) Power Failure
- Q.7 Class A-Chopper operates in (CO3)  
 a) First quadrant  
 b) Second quadrant  
 c) All four quadrants  
 d) Both first and second quadrant
- Q.8 MOSFET is a (CO1)  
 a) Current controlled device  
 b) Voltage controlled device  
 c) Both A & B  
 d) Power controlled device
- Q.9 SCR is a \_\_\_\_\_ layer and \_\_\_\_\_ terminal device. (CO1)  
 a) 3,3 b) 4,4  
 c) 4,3 d) 3,4
- Q.10 A 3 phase full wave fully controlled converter is a \_\_\_\_\_ pulse converter. (CO2)  
 a) 3 b) 6  
 c) 12 d) 2

### SECTION-B

- Note:** Objective type questions. All questions are compulsory. (10x1=10)
- Q.11 The value of latching current is more than Holding Current. (True/False) (CO1)

- Q.12 SCR is a Fully Controlled Switch?(True/False) (CO1)
- Q.13 The three terminals of SCR are Gate. Drain and Source. (True/False) (CO1)
- Q.14 The cathode of the SCR is always at negative potential w.r.t. anode (True/False) (CO1)
- Q.15 A UJT has \_\_\_\_\_ PN junction. (CO1)
- Q.16 A rectifier converts \_\_\_\_\_ to \_\_\_\_\_. (CO2)
- Q.17 The full form of UPS is \_\_\_\_\_. (CO5)
- Q.18 What is firing angle? (CO2)
- Q.19 What is slip power? (CO3)
- Q.20 Give applications of dual converter? (CO3)

### SECTION-C

- Note:** Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)
- Q.21 What is an inverter? What are its different types? (CO3)
- Q.22 Explain the controlling techniques of the chopper? (CO3)
- Q.23 Explain the working of SMPS with diagram. (CO3)
- Q.24 Explain different types of choppers according to quadrants. (CO3)
- Q.25 Explain the following terms related to SCR. (CO1)  
 a) Forward break over voltage  
 b) Latching current c) Holding current  
 d) Forward dv/dt rating e) PIV rating
- Q.26 Explain the UJT relaxation oscillator with diagram. (CO1)
- Q.27 What are AC and DC drives? (CO1)