

- Q.28 Define power factor and its importance. (CO-6)
- Q.29 State the maximum power transfer theorem. Show that for maximum power transfer when $R_1 = R_{TH}$. (CO-2)
- Q.30 Draw and explain the B-H loop. (CO-4)
- Q.31 Describe the basis features of balanced 3 phase system. (CO-8)
- Q.32 Determine phase angle relationship between alternating voltage and current in a purely inductive circuit. (CO-7)
- Q.33 Derive an expression for the energy stored in the magnetic field of a coil possessing an inductance of L. Henry when the current flowing through it is lamperes. (CO-6)
- Q.34 Derive an expression for the instantaneous value of alternating voltage varying sinusoidally. (CO-7)
- Q.35 Explain the charging method for lead acid accumulator. (CO-3)

SECTION-D

- Note:** Long answer type questions. Attempt any two out of three questions. (2x10=20)
- Q.36 Drive the relationship between line voltage and line current with phase voltage and phase current in Death connected circuit. (CO-8)
- Q.37 Explain Real Power. Reactive Power and Apparent Power with the help of Power triangle in case of RLC series circuit. (CO-7)
- Q.38 Explain the hysteresis loop and hystersis Loss. (CO-4)

No. of Printed Pages : 4

170932/030932

Roll No.

3rd Sem. / Electrical GE, Power Station Engg., Elect. & Eltx. Engg.

Subject : Fundamentals of electrical Engineering

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice Questions. All questions are compulsory (10x1=10)

- Q.1 The form factor is the ratio of (CO-7)
- Average value to rms value
 - rms value to average value
 - Peak value to average value
 - Peak value to rms value
- Q.2 A current is said to be alternating when it changes in (CO-7)
- Magnitude only
 - Direction only
 - Both magnitude and direction
 - None of the above
- Q.3 The unit of electrical energy is (CO-5)
- Watt-sec
 - Joule
 - kWh
 - All of the above
- Q.4 Area of hysteresis loop represents (CO-4)
- Copper loss
 - Eddy current loss
 - Hysteresis loss
 - Iron loss

- Q.5 The resistance of wire varies inversely as (CO-1)
- Area of cross-section
 - Length
 - Resistivity
 - Temperature
- Q.6 Thevenin's resistance R_{TH} is determined (CO-2)
- By short-circuiting the given two terminals
 - By removing the voltage sources along with their internal resistance
 - Between same open terminals as for V_{TH}
 - Between any two open terminals
- Q.7 The frequency of an alternating quantity is (CO-7)
- The speed with which the alternator runs
 - The number of direction reversals in per second
 - The number of cycles completed per second
 - The number of cycles completed per minutes
- Q.8 Cells are connected in series in order to increase the (CO-3)
- Current capacity
 - Life of the cells
 - Voltage rating
 - Terminal voltage
- Q.9 In a 3-phase, balanced load, the power consumed is given by the relation. (CO-8)
- $\sqrt{3} V_L I_L \cos \Phi$
 - $3 V_{PH} I_{PH} \cos \Phi$
 - Both (a) and (b)
 - None of the above
- Q.10 In two-wattmeter method of 3-phase power measurement in balanced load having 0.5 p.f. lagging. (CO-8)
- One wattmeter reads zero
 - One wattmeter reads down scale
 - Both the wattmeters read equally
 - Both the wattmeters give equal but opposite readings.

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 Define voltage and its unit. (CO-5)
- Q.12 Draw a parallel circuit having three resistances R_1 , R_2 and R_3 connected across a supply voltage V volt. (CO-8)
- Q.13 Define Secondary cell with one example. (CO-7)
- Q.14 Define eddy current. (CO-2)
- Q.15 Define phase. (CO-7)
- Q.16 Write the unit of frequency? (CO-7)
- Q.17 Give the unit of Inductive reactance. (CO-4)
- Q.18 Weber is the SI unit of _____. (CO-5)
- Q.19 All the domestic appliances are connected in _____ with the circuit. (CO-2)
- Q.20 Draw a phasor diagram of R-C series circuit. (CO-4)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain series and parallel connection of inductances. (CO-1)
- Q.22 Differentiate between primary and secondary cells. (CO-3)
- Q.23 Differentiate between AC and DC? (CO-4)
- Q.24 State the Faraday's Law's of Electro magnetic induction. (CO-7)
- Q.25 State and explain the Thevenin's theorem. (CO-4)
- Q.26 List five uses of electrical energy. (CO-6)
- Q.27 State Kirchhoff's Voltage law and current law? (CO-2)