

- Q.26 Discuss about the single phase half wave controlled rectifier with load.
- Q.27 Write a short note on single phase semi-converter.
- Q.28 What is a chopper & explain its different types in detail.
- Q.29 What is cycloconverter & what are its applications.
- Q.30 What is electric drive & explain with the help of block diagram of an electric drive system.
- Q.31 What is UPS & Explain ON line UPS.
- Q.32 What is the need of freewheeling Diode.
- Q.33 Mention disadvantages of AC devices over DC derives.
- Q.34 Write a short note on Heat Sinks.
- Q.35 Explain the working of Dual Converter.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain the construction & working of SCR also draw explain the VI characteristics.
- Q.37 Write a short notes on any two of the following :-
- Series & parallel operation of SCR
 - GTO
 - MOSFET
- Q.38 Explain all types of choppers in details.

No. of Printed Pages : 4

181551/121551/073651

Roll No.

5th Sem / IC, EI Subject:- Power Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 A light activated SCR is a :-
- Too layer two junction device
 - Two layer three junction device
 - Four layer three junction device
 - Four layer two junction device
- Q.2 The most commonly used method for firing as SCR is:-
- Radiation Triggig Process
 - Gate Triggering Process
 - Voltage Triggering Process
 - Thermal Triggering Process
- Q.3 The minimum gate current which can term on SCR is called:
- Trigger current
 - Holding current
 - Break over current
 - None of the above
- Q.4 SCR can be used as ____.
- Uni-directional
 - Bi-directional

- c) Both A & B
d) None of the above
- Q.5 A 3 Phase fully controlled converter is a
a) 3 Pulse converters b) 6 Pulse converters
c) 2 Pulse converters d) 12 Pulse converters
- Q.6 The voltage of a controlled rectifier output is maximum when firing angle is-
a) 120° b) 60°
c) 0° d) 90°
- Q.7 An Cycloconverter is a :-
a) AC-DC Converter b) DC-AC Converter
c) DC-DC Converter d) AC to AC Converter
- Q.8 Average output of a DC Chopper is given by
a) $V_o = \frac{V_s}{a}$ b) $V_o = \frac{a}{V_s}$
c) $V_o = V_s \times \alpha$ d) None of these
- Q.9 Variable Voltage fixed frequency supply is obtained by:
a) Three Phase Inverter
b) Three Phase Cycloconverter
c) AC Chopper
d) Dual Converter
- Q.10 UPS is used in
a) Computers
b) Communication links
c) Essential Instrumentation
d) All of these

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 With the increase in firing angle of SCR output is increased (True/False)
- Q.12 A UJT has _____ PN junction.
- Q.13 What is Holding current.
- Q.14 Define Triggering.
- Q.15 Define MOSFET
- Q.16 Draw the symbol of DIAC
- Q.17 Difference between controlled & uncontrolled rectifier.
- Q.18 What is an inverter?
- Q.19 What do you mean by electric drive.
- Q.20 What is UPS?

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Write about the SCR specifications & ratings.
- Q.22 Discuss about the different methods of SCR triggering.
- Q.23 Discuss about the parallel operation of SCR.
- Q.24 Draw V-I characteristics of TRIAC & draw the diagram also.
- Q.25 Discuss about the different commutational ckt of SCR.