

Roll no. _____

ID: 220824

Semester: 2nd

Branch: Computer

Subject Name: Analog Electronics

Time Allowed : 3 Hrs.

MM: 60

Section –A

Note: Multiple Choice questions. All questions are compulsory.

6x1=6

- Q.1 FET is a _____ device.
- | | |
|--------------|--------------|
| (a) Tripolar | (b) Unipolar |
| (c) Bipolar | (d) None |
- Q.2 Addition of pentavalent impurity to a semiconductor creates many _____.
- | | |
|---------------------|--------------------|
| (a) Free electrons | (b) Holes |
| (c) Valence charged | (d) Bound electron |
- Q.3 in a NPN transistor the emitter current is mainly due to _____.
- | | |
|-------------|---------------|
| (a) Holes | (b) Electrons |
| (c) Protons | (d) None |
- Q.4 Complementary PUSH PULL amplifier uses _____ amplifiers.
- | | |
|----------|----------|
| (a) Two | (b) One |
| (c) Four | (d) None |
- Q.5 A semiconductor has _____ temperature coefficient of resistance.
- | | |
|--------------|-----------------------|
| (a) Positive | (b) Negative |
| (c) Zero | (d) None of the above |
- Q.6 For highest power gain, we use _____ transistor configuration
- | | |
|--------|--------|
| (a) CA | (b) CC |
| (c) CB | (d) CE |

Section-B

Note: Objective/Completion type questions. All questions are compulsory. **6x1=6**

- Q.7 Expand FET.
- Q.8 What is regulator?
- Q.9 What is Integrator circuit?
- Q.10 What is multivibrator?
- Q.11 What is Heat Sink?
- Q.12 What is Donor impurities?

Section –C

Note: Short answer type Questions. Attempt any eight questions out of ten questions. **8x4= 32**

- Q.13 Explain reverse bias characteristics of Zener diode.
- Q.14 Explain difference between Intrinsic and Extrinsic Semiconductor.
- Q.15 Explain the working of N type enhancement mode MOSFET.
- Q.16 Explain relation between alpha and beta.
- Q.17 Explain working of 7805.
- Q.18 Explain OP-AMP as differentiator.
- Q.19 Explain low pass and high pass active filters.
- Q.20 Explain thermal runaway and stabilization.
- Q.21 Explain half wave rectifier working.
- Q.22 What is feedback and advantages of negative feedback?

Section-D

Note: Long answer questions. Attempt any two questions out of three questions.

2x8=16

- Q.23 Explain timers and its block diagram and its PIN diagram.
- Q.24 Explain working of Class A amplifier with its advantages and disadvantages.
- Q.25 Explain transistor as a switch and give applications of FET.