

- Q.26 What is a DC load line? What is its importance?
- Q.27 Write the comparison between BJT and JFET.
- Q.28 Differentiate between N-Type and P-Type extrinsic semiconductor.
- Q.29 Why capacitors are connected in parallel and inductor in series in filter circuits?
- Q.30 Explain Schottky diode.
- Q.31 Explain the energy band structure of Si & Ge.
- Q.32 Draw and explain the atomic structure of P-Type semiconductor.
- Q.33 Discuss the working of single stage amplifiers in CE configuration.
- Q.34 Explain the working of half wave rectifier with suitable waveforms.
- Q.35 Draw the characteristics of zener diode and explain it.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Compare CB, CC and CE configurations.
- Q.37 Draw the circuit diagram of full wave bridge rectifier and explain its working along with waveforms.
- Q.38 Differentiate semiconductor, conductor and insulator on the basis of energy band structure. Why semiconductors have negative temperature coefficient of resistance?

No. of Printed Pages : 4

120933/030933

Roll No.

**3rd Sem / Electrical Engg., GE, Power Station Engg.,
Elect. & Eltx. Engg., Fire Tech & Safety
Sub : Electronics – I/Basic Electronics**

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 Diffusion capacitance depends on
a) Area of junction
b) Permittivity
c) Width of depletion region
d) Mean lifetime of carriers
- Q.2 Which of the following is not a semiconductor?
a) Lead b) GaAs
c) Silicon d) Germanium
- Q.3 The value of forbidden energy gap in insulators is of the order of
a) 0 eV b) 1 eV
c) 5 eV d) Less than 2 eV
- Q.4 The biasing circuit which gives best stability to Q-point is
a) Emitter resistor biasing
b) Potential divider biasing
c) Feedback resistor biasing
d) Base resistor biasing

- Q.5 The functions of emitter in NPN transistor is
- To emit or inject holes into collector
 - To emit or inject electrons into collector
 - To emit or inject electrons into base
 - To emit or inject holes into base
- Q.6 A field effect transistor is essentially a
- Current driven device
 - Voltage driven device
 - Power driven device
 - None of the above
- Q.7 In case of ideal current sources, they have
- Large value of current
 - Low value of voltage
 - Zero internal resistance
 - Infinite internal resistance
- Q.8 What is Zener diode used as?
- Regulator
 - Oscillator
 - Filter
 - Rectifier
- Q.9 JFET is a _____ controlled device
- Resistance
 - Proton
 - Current
 - Voltage
- Q.10 The purpose of coupling capacitor in an amplifier is to
- Control frequency
 - Match impedance
 - Limit bandwidth
 - Prevent DC mixing with output

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 What is the purpose of transistor in electronic circuits?
- Q.12 Capacitance can be defined as the ratio of electric charge on each conductor to what between them?
- Q.13 What are multistage amplifiers?
- Q.14 What is JFET?
- Q.15 Draw PNP transistor.
- Q.16 Give graphical representation of current source
- Q.17 The number of diodes required in a bridge rectifier circuit is/are _____.
- Q.18 What is the value of ripple factor of full wave rectifier?
- Q.19 What type of device is a diode?
- Q.20 Why the stabilization of operating point is needed?

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Deduce the relation between **a**, **b** and **g**.
- Q.22 What are filter circuits? Explain any one filter circuit.
- Q.23 What are parameters? Why are they used?
- Q.24 Give the characteristics of a MOSFET.
- Q.25 Draw the frequency response of single stage transistor amplifier.