

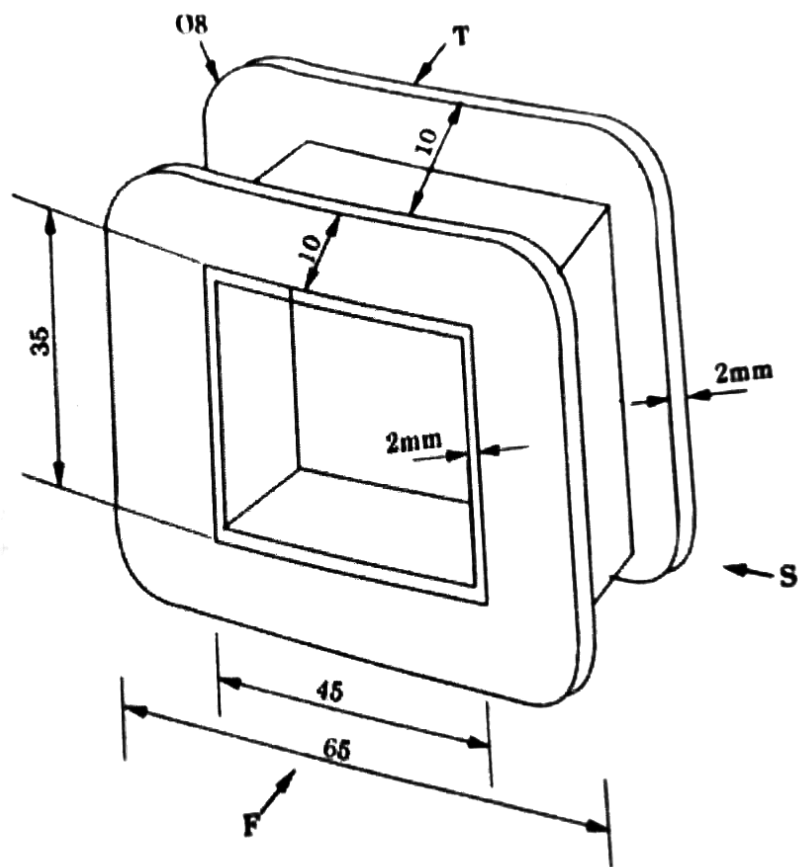


Fig:2

No. of Printed Pages : 2

Roll No.

180934/170934/

120934/030934

**3rd Sem /Electrical Engineering,
Power Station Engg., Elect. & Eltx. Engg.
Sub : Electrical Engineering Design & Drawing-I**

Time : 3Hrs.

M.M. : 100

SECTION-A

(10x2=20)

Q.1 Draw any ten symbols of following

- i) Double pole MCB
- ii) Ceiling fan
- iii) Energy meter
- iv) Symbol of resistor
- v) Bell
- vi) Capacitor
- vii) Female plug IEC system
- viii) Fuse
- ix) Inductor
- x) Postive Polarity
- xi) Battery
- xii) Transformer

(400)

(4)

180934/170934/
120934/030934

(1)

180934/170934/
120934/030934

SECTION-B

Note: Attempt any two questions out of three questions.
(20x2=40)

- Q.2 Draw the single line schematic and wiring diagram of two lamps control by two switches.
- Q.3 Design the wiring diagram for staircase lighting circuit.
- Q.4 Design and draw single line and wiring diagram of distribution panel for industrial building. The electrical circuit consists of energy meter, main switch and ELCB.

SECTION-C

Note: Attempt any one questions out of two questions.
(40x1=40)

- Q.5 Isometric view & orthographic views of a bus bar post are shown in Fig 1. Draw the following views to a suitable scale:
- Front view right half in section
 - Top view

- Q.6 Draw front view, side view and top view of fig 2 show isometric view of bobbins of a small transformer.

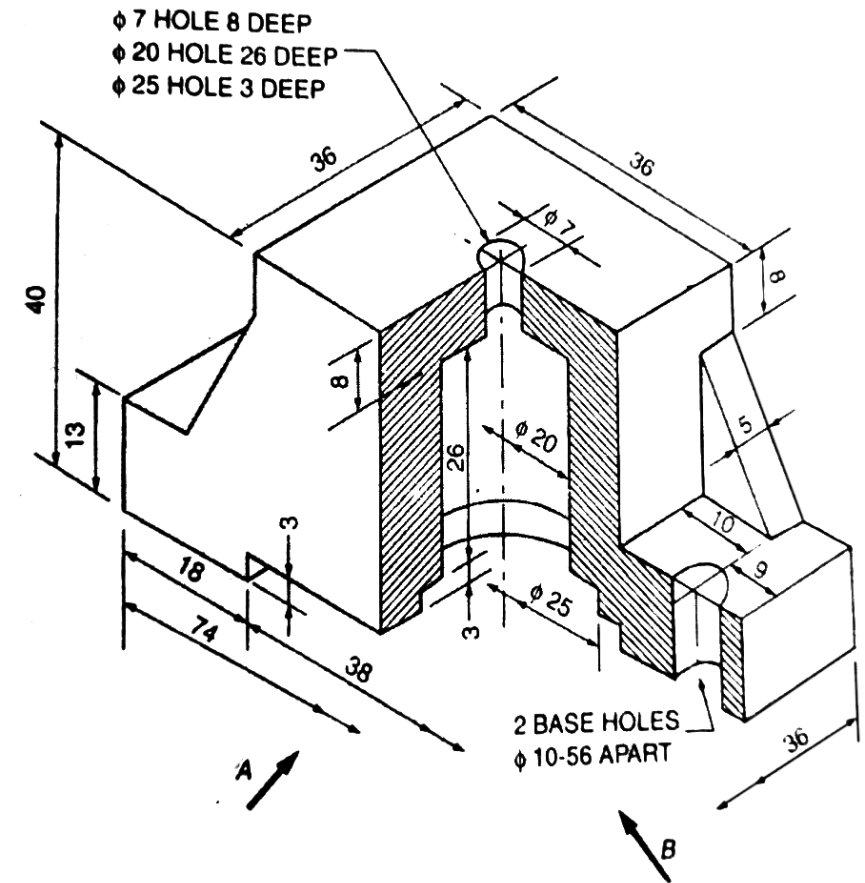


Fig.1

(2)

180934/170934/
120934/030934

(3)

180934/170934/
120934/030934