

- Q.25 Draw and explain the waveforms of a single-phase fully controlled bridge rectifier.
- Q.26 Explain the working of a series inverter with circuit diagram and waveforms.
- Q.27 Describe the types of chopper with their applications.
- Q.28 Explain the working principle of cycloconverter and what are its applications?
- Q.29 Explain the working of single phase full wave converter drive.
- Q.30 Draw and explain the circuit diagram of step up chopper.
- Q.31 Write short note on “Dual converter”.
- Q.32 Define Electric drives. Write any two disadvantages of AC drive over DC drive.
- Q.33 What are the different types of batteries used in UPS system? Discuss their classification.
- Q.34 Explain the construction and working principle of TRIAC with their V-I characteristics.
- Q.35 How a GTO is different from an SCR? Explain the comparison of SCR and GTO.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain different methods of SCR triggering.
- Q.37 Explain the different types of UPS systems. Discuss the working principle of each type and compare their advantages and disadvantages.
- Q.38 Explain with the help of suitable diagram for automatically control the speed of a DC shunt motor.

(520)

(4)

181043/171043

No. of Printed Pages : 4

181043/171043

Roll No.

4th Sem / Eltx

Subject:- Power Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 ADIAC is used to:
- Commutate a TRIAC
 - Trigger a TRIAC
 - To protect a TRIAC
 - All of the above
- Q.2 The primary functions of an SCR in a power electronics circuit:
- Voltage control
 - Current control
 - Power amplification
 - Switching device
- Q.3 UJT is a :
- Current controlled device
 - Voltage controlled device
 - A relaxation oscillator
 - All of the above
- Q.4 A fully controlled rectifier circuit contains:
- Only SCRs
 - Only diodes
 - Mixture of SCRs and diodes
 - None of the above

(1)

181043/171043

- Q.5 The duty cycle of a chopper is:
 a) Ton/Toff b) Toff/Ton
 c) Ton / (Ton + Toff) d) Toff/ (Ton + Toff)
- Q.6 Cycloconverter drives are generally employed in;
 a) Traction
 b) Milling
 c) Generating low frequencies
 d) Generating pulses
- Q.7 The TRIAC is equivalent to:
 a) Two SCRs connected in parallel
 b) Two SCRs connected in anti parallel
 c) One SCR, one diode connected in parallel
 d) One diode, one SCR connected in anti parallel
- Q.8 In AC drive control, the purpose of constant V/F operation is:
 a) To maintain constant voltage
 b) To maintain a constant frequency
 c) To provide smooth control of motor speed
 d) To achieve high efficiency
- Q.9 A UPS consists of:
 a) Battery charger b) Inverter
 c) Battery d) All of the above
- Q.10 High-voltage DC transmission is used because:
 a) It is costlier
 b) It reduces line losses
 c) It requires more transmission towers
 d) It reduces power efficiency

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 AUJT has _____ PN junction.
- Q.12 The turn on time of an SCR is about 2 to 5 μ s (True/False)
- Q.13 To turn off an SCR, it is necessary to reduce its current to less than trigger current. (True/False)
- Q.14 The output voltage of a controlled rectifier is controlled by controlling _____ of thyristor.
- Q.15 Lead acid batteries are costlier than SMF batteries. (True/False)
- Q.16 Class-D chopper operates in _____ quadrants.
- Q.17 A cycloconverter consist of _____ and _____ group of thyristors.
- Q.18 In a dual converter one converter operates as _____ and other _____.
- Q.19 In ON-line UPS, the inverter is _____ all the time.
- Q.20 UPS is never used in street lighting. (True/False)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain the working of an of SCR with the help of two transistor analogy.
- Q.22 Write any five V-I characteristics of UJT.
- Q.23 Define and explain the construction and working principle of DIAC.
- Q.24 Explain the operation of single phase half-wave controlled rectifier with waveforms.