

Roll No.

/170832/120832/030832

**3rd Sem / Computer, ECE, Automation & Robotics ,
Computer (For Speech and Hearing Impaired),
ECE (For Speech and Hearing Impaired) , IT, Eltx,
EI, , Med. Eltx., Power Eltx, Elect. & Eltx. Engg**

**Subject : Digital Electronics / Digital Eltx.- I /
Digital Electronics & Computer Architecture**

M.M. : 60

Note: Multiple choice questions. All questions are compulsory (6x1=6)

a) 1110 b) 1100
c) 1111 d) 1001

- Detect errors
- Convert decimal to binary
- Simplify addition
- Minimize errors during transitions

a) All inputs are 0 b) At least one input is 1
c) All inputs are 1 d) None of the above

(1) 220832/212832/180832
/170832/120832/030832
/031034/106544

- Q.4 D flip-flop is also called:
- a) Data or Delay flip-flop
 - b) Direct flip-flop
 - c) Differential flip-flop
 - d) Double flip-flop
- Q.5 Universal shift register can:
- a) Only shift left
 - b) Only shift right
 - c) Shift in both direction
 - d) Only store data
- Q.6 Which memory can be erased by UV light?
- a) PROM
 - b) EPROM
 - c) RAM
 - d) EEPROM

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 PROM_____.
- Q.8 What is the symbol of XOR gate?
- Q.9 Name any two logic gate.
- Q.10 Name two types of counters.
- Q.11 What is the function of an encoder?
- Q.12 What is a flip-flop?

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 What is parity? Explain single and double parity.

(2) 220832/212832/180832
/170832/120832/030832
/031034/106544

- Q.14 Write differences between TTL and CMOS logic families.
- Q.15 Explain the working of half adder.
- Q.16 What is demultiplexer? Design 16:1 Demultiplexer.
- Q.17 Explain Decimal to BCD encoder with block diagram.
- Q.18 Differentiate between Latches and Flip-Flop.
- Q.19 Explain the performance characteristics of digital to analog convertor.
- Q.20 Write short note on
- a) RAM
 - b) ROM
- Q.21 Compare synchronous and asynchronous counter.
- Q.22 Write a short note on Excess-3 code and gray code.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 What do you mean by multiplexer? Design 32:1 MUX by using 16:1 MUX and 2:1 Mux
- Q.24 Write short note on any two
- a) latch
 - b) Encoder
 - c) Universal shift register
- Q.25 Explain the working of master slave J-K flip-flop. How it will overcome the race around condition of flip-flop.

(1740)

(4) 220832/212832/180832
/170832/120832/030832
/031034/106544