

Q.22 The complementary symmetry push-pull amplifiers are called so why?

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

Q.23 What is Multistage Amplifier? Explain the working of transformer coupled amplifier. with the help of its circuits diagram. (3+5)

Q.24 What are single and double tuned voltage amplifiers? Draw frequency response characteristics of double tuned voltage amplifier. (6+2)

Q.25 a) Write short note on Push-pull amplifier. (4)
b) Define CMRR and slew rate. (2+2)

No. of Printed Pages : 4 221034/181031/171031
Roll No. /121031/031031

3rd Sem / ECE, ECE, (For Speech and Hearing Impaired), Eltx, Mecatronics, Med, Eltx, Power Eltx, Elect. & Eltx. Engg.

**Subject : Electronic, Devices and Circuits. - II /
Electronic Devices and Circuits/ Analog Eltx- II**

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

Q.1 The frequency response of transformer coupling is

a) Good b) Very Good

c) Excellent d) Poor

Q.2 What is the purpose of RC or transformer coupling?

- a) To block a.c.
- b) To separate bias of one stage from another
- c) Increase thermal stability
- d) Increase Efficiency

Q.3 What does class A amplifier do?

a) Delivers KV of voltage to load

(1800) (4) 221034/181031/171031
/121031/031031

(1) 221034/181031/171031
/121031/031031

- b) Delivers KW of power
- c) Delivers Kilo pascal pressure
- d) Delivers more resistance

Q.4 What are oscillators?

- a) Switching circuits b) Converts dc to ac
- c) Converts ac to dc d) Filter circuits

Q.5 A multivibrator is an electronic circuit used to implement _____

- a) Oscillator b) Timer
- c) Flip-Flop d) All of the mentioned

Q.6 Which factor determines the gain of the voltage series feedback amplifier?

- a) Open loop voltage gain
- b) Feedback voltage
- c) Ratio of two resistors
- d) Gain of feedback circuit

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

Q.7 An ideal range signal amplifier delivers 100% DC power to its load. (True/False)

(2) 221034/181031/171031
/121031/031031

Q.8 Positive feedback is also called _____

Q.9 Define voltage gain.

Q.10 741 is _____ pin IC.

Q.11 Op-Amp is short form of _____

Q.12 Balancing type feedback is also called as _____.

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

Q.13 What is the need for multistage amplifier.

Q.14 Draw circuit diagram of emitter follower amplifier and write any two applications of it. (3+1)

Q.15 Write the basic parameters of Op-amp

Q.16 Differentiate between voltage and power amplifier.

Q.17 Draw pin diagram of IC 555.

Q.18 Explain importance of impedance matching in amplifier.

Q.19 Draw pin-diagram of IC-741 and explain its pin configuration.

Q.20 Define positive and negative feedback?

Q.21 Explain the working of Hartley oscillator.

(3) 221034/181031/171031
/121031/031031