

- Q.4 A step up chopper can give on output voltage (CO3)
 a) higher than input voltage
 b) lower than input voltage
 c) both higher and lower input voltage
 d) all of above
- Q.5 Armature control method is used in DC motor to get (CO4)
 a) constant speed
 b) Speed above normal speed
 c) speed below normal speed
 d) Both B & C
- Q.6 UPS stands for (CO5)
 a) Unipolar Power supply
 b) Uninterrupted Polar supply
 c) Uninterrupted Power supply
 d) None of the above

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 The method of switching off a thyristor is known as its _____ (CO1)

(2) 222831/212831

- Q.8 The holding current of a thyristor is _____ than the latching current. (CO1)
- Q.9 The output voltage of a controlled rectifier is controlled by controlling _____ of thyristor. (CO2)
- Q.10 A inverter converts _____ into _____. (CO3)
- Q.11 The speed of the motor increase in the increase in _____. (CO4)
- Q.12 SMPS stands for _____. (CO5)

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 Explain the different methods of triggering of an SCR. (CO1)
- Q.14 Explain the battery charger circuit using SCR with diagram. (CO1)
- Q.15 Explain the single phase half wave controlled rectifier with resistive and inductive load. (CO2)
- Q.16 Explain the application of Dual convertor. (CO1)
- Q.17 Explain the series inverter with the help of diagram. (CO3)
- Q.18 What are the advantages and disadvantages of AC drives. (CO4)
- Q.19 Explain the working of DC Chopper drive in Regenerative Braking mode. (CO4)

(3) 222831/212831