

Draw the Front View,, side and top view of transformer bobbin as shown in fig 2

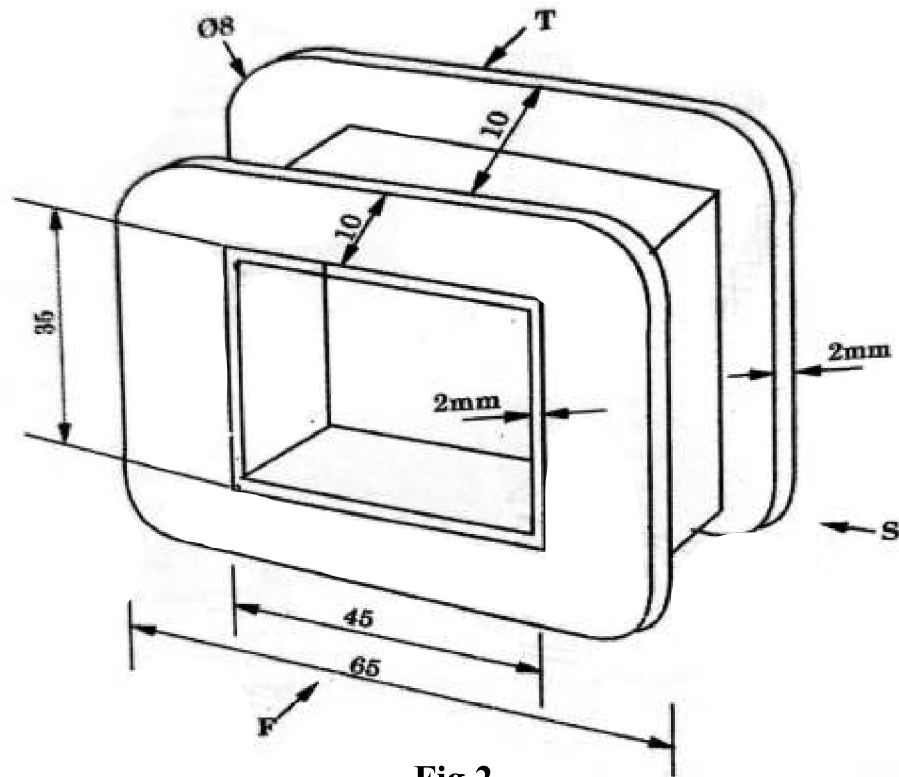


Fig.2

- Dimension units may be taken in mm.
- Assume suitable dimensions as required if not specified or not visible clearly in the figure

No. of Printed Pages : 4 180934/170934/120934
Roll No. /030934

3rd Sem / Electrical, Power Station Engg.,
Elect. & Eltx. Engg.

Subject : Electrical Engineering Design and Drawing -I

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Very Short Answer type questions. Attempt all 15 parts.
(15x2=30)

Q.1 Draw the symbols of

- Earth electrode
- TPIC
- HRC Fuse
- Fire Indicator
- Main switch power
- Two way switch
- Loud speaker
- Siren
- Dc motor
- Energy meter

(1560)

(4) 180934/170934/120934
/030934

(1) 180934/170934/120934
/030934

- xi) Voltmeter
- xii) Moving iron instrument
- xiii) Bell
- xiv) Heater
- xv) Fan regulator

SECTION-B

Note: Attempt all ten Questions.

Q.2 Draw the schematic and wiring diagram for controlling one light, one fan with regulator, one bell and one 6 Amp socket (with earth terminal) to be controlled by individual switches. 20 (CO 3&4)

OR

Draw the schematic, wiring and single line diagram for single stair case wiring system by using appropriate switches.

Q.3 Draw the wiring diagram and single line diagram of a house showing Energy meter, Main switch, ELCB, two distribution board 04 sub circuit on one distribution board while 03 on another distribution board and also show one fan one light one 6amp socket on one sub circuit. 20(CO5)

(2) 180934/170934/120934
/030934

Q.4 Draw the assembled view of pin type insulator shown in fig 1 (CO6) 30

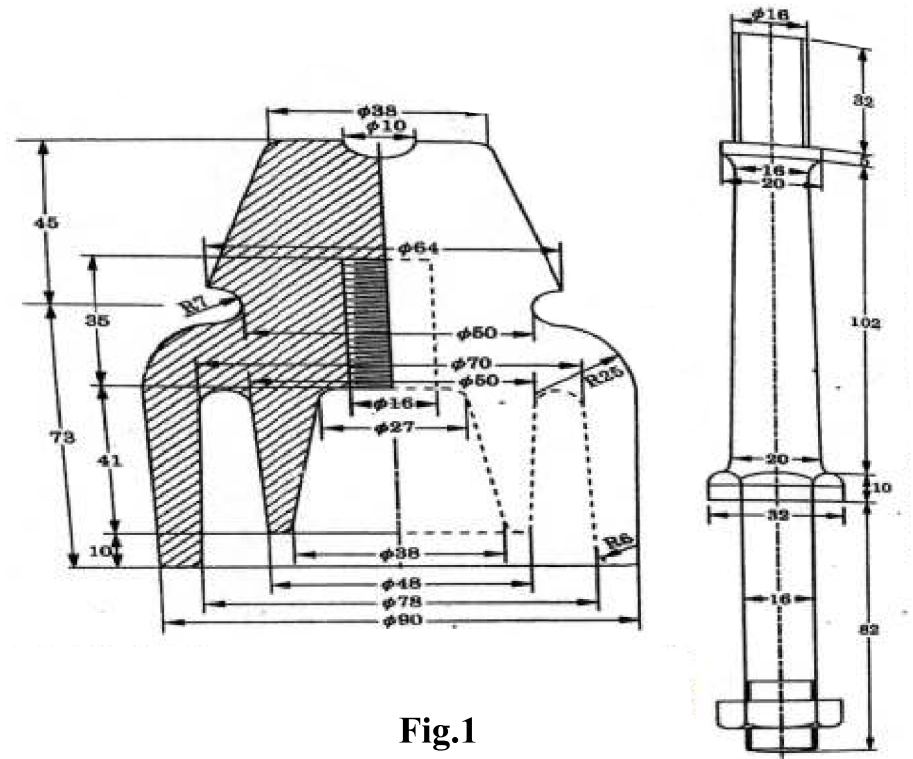


Fig.1

- Dimension units may be taken in mm.
- Assume suitable dimensions as required if not specified or not visible clearly in the figure

OR

(3) 180934/170934/120934
/030934