

- Q.30 Explain the series and parallel combination of resistance with circuit diagram. (CO4)
- Q.31 Write the care and maintenance of lead acid batteries. (CO3)
- Q.32 Difference between electrical and magnetic circuits. (CO6)
- Q.33 Explain the Fleming's right hand rule. (CO5)
- Q.34 What is the power factor in AC circuits? State disadvantage of low power factors. (CO7)
- Q.35 Discuss about parallel resonance in AC circuit. (Co7)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain Thevenin Theorem and its use in electric circuit. (CO2)
- Q.37 State and explain Faraday's law of electro-magnetic induction. (CO4)
- Q.38 Explain the construction, principle and working of lead-acid battery. (CO5)

No. of Printed Pages : 4

Roll No.

202425/171027/

120828/030828

**2nd Semester/ Comp, ECE, IT, I & Control, Med,
Eltx, Eltx & Instr., Power Eltx, EEE
Subject : Basic Electrical Engineering**

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 Internal resistance of ideal voltage source is (CO3)
- a) Zero b) Infinite
- c) Very Low d) Very High
- Q.2 The frequency of DC is (CO6)
- a) Zero b) 50
- c) 100 d) Infinite
- Q.3 The number of cycles completed in one second is called (CO6)
- a) Time Period b) Voltage
- c) Frequency d) None of above
- Q.4 The unit of current is (CO1)
- a) Ampere b) Volt
- c) Watt d) None of these

- Q.5 Power factor for pure inductive load is (CO3)
 a) Unity b) Zero
 c) Lagging d) None of these
- Q.6 The unit of inductance is (CO7)
 a) Ohm b) Watt
 c) Volt d) Henry
- Q.7 Unit of flux density is (CO4)
 a) Henry b) Weber / m²
 c) Joule d) None of the above
- Q.8 The rate of doing work is called (CO1)
 a) Power b) Current
 c) Voltage d) None of these
- Q.9 The energy meter measures the energy in (CO2)
 a) Watts b) KWH
 c) Megawatts d) Kilowatts
- Q.10 The solar cell converts solar energy into _____ (CO5)
 energy.
 a) Chemical b) Mechanical
 c) Electrical d) None of above

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (10x1=10)

- Q.11 Insulators have __ resistance. (CO1)

(2)

202425/171027/
120828/030828

- Q.12 Define KCL? (CO2)
- Q.13 What is mutual induction? (CO4)
- Q.14 What is the unit of capacitance? (CO3)
- Q.15 Define Susceptance. (CO1)
- Q.16 What are passive components? (CO1)
- Q.17 In a circuit power is measured by _____. (CO2)
- Q.18 The device which converts DC into AC is called _____. (CO1)
- Q.19 Unit of conductance is _____. (CO4)
- Q.20 What is the full form of EMF? (CO5)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain maximum power transfer theorem? (CO2)
- Q.22 Discuss concept of Ideal Current Source. (CO3)
- Q.23 Give significance to the power factor. (CO7)
- Q.24 Explain Kirchhoff voltage law. (CO1)
- Q.25 What is a cell? Explain its types. (CO5)
- Q.26 Difference between a.c. and d.c. (CO1)
- Q.27 What is Resonance? Explain series resonance in detail. (CO3)
- Q.28 Explain the working of solar cell. (CO5)
- Q.29 Define flux and reluctance. (CO4)

(3)

202425/171027/
120828/030828