

- Q.27 Define chopper. What are different types of choppers. (CO3)
- Q.28 Write the advantages of HVDC transmission. (CO5)
- Q.29 Draw and explain the circuit diagram of dual converter. (CO4)
- Q.30 Explain the circuit diagram of motor drive control. (CO5)
- Q.31 Explain the circuit diagram of offline UPS. (CO5)
- Q.32 Write down the merits and demerits of series inverter. (CO4)
- Q.33 Explain the function of freewheeling diode. (CO2)
- Q.34 Discuss the applications of cyclo-converter. (CO4)
- Q.35 Explain Voltage source inverter. (CO5)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Define triggering of SCR. Explain different types of triggering methods. (CO2)
- Q.37 Differentiate between online, offline and line interactive inverter. (CO4)
- Q.38 Write short note on any two
- V-I Characteristics of SCR
 - Constant V/F operation AC drive control
 - Fully controlled full wave bridge rectifier.

No. of Printed Pages : 4
Roll No.

202451

5th Semester/ Mechatronics Subject : Power Electronics

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 An SCR is a ___ layer device (CO1)
- 2
 - 4
 - 3
 - 5
- Q.2 A TRIAC is a ___ device (CO1)
- Unidirectional
 - Bidirectional
 - Both
 - None
- Q.3 The process of Turn ON of an SCR is called _____. (CO2)
- Triggering
 - Commutating
 - Blocking
 - None of the above
- Q.4 If firing angle of an SCR circuit is decreased, the output _____. (CO2)
- Remains the same
 - Is increased
 - Is decreased
 - None of the above
- Q.5 _____ device/s can be used in a chopper circuit. (CO3)
- BJT
 - MOSFET
 - GTO
 - All of the above

- Q.6 A single phase full wave half controlled rectifier uses _____. (CO2)
 a) 2 SCRs b) 3 SCRs
 c) 4 SCRs d) 6 SCRs
- Q.7 The main advantage of SMPS over linear power supply? (CO5)
 a) No transformer is required
 b) Higher efficiency
 c) No filter required
 d) Only one state of conversion
- Q.8 A cyclo converter having negative half of load current is carried by _____. (CO4)
 a) Negative converter only
 b) Positive converter only
 c) Positive & Negative converter
 d) Positive or negative converter
- Q.9 A PWM switching scheme is used in single phase inverters to: (CO4)
 a) Reduce the higher order harmonics
 b) Minimize the effect of load.
 c) Reduce the lower order harmonics
 d) Reduce the total harmonic distortion
- Q.10 UPS stands for _____. (CO5)
 a) Universal power supply
 b) Uninterruptive power supply
 c) Universal power system
 d) None of the above

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (10x1=10)

- Q.11 SUS stands for _____. (CO1)
- Q.12 Controlled Rectifier contains only diodes. (True/False) (CO2)
- Q.13 Define dv/dt triggering? (CO2)
- Q.14 The duty cycle of chopper is expressed by _____. (CO3)
- Q.15 Write the terminal name of UJT. (CO1)
- Q.16 _____ active material used for positive plate of lead acid battery. (CO3)
- Q.17 HVDC stands for _____. (CO5)
- Q.18 Freewheeling diode is used to improve power factor in controlled rectifiers. (True/False) (CO2)
- Q.19 The most suitable motor for control application is _____ motor. (CO5)
- Q.20 Which motor is used for elevators? (CO5)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Describe the two transistor model of SCRs. (CO1)
- Q.22 Explain Class B commutation method of SCR. (CO2)
- Q.23 Explain the working principle of UJT. (CO2)
- Q.24 Write any four specifications of SCR. (CO1)
- Q.25 Draw the circuit diagram battery charger using thyristor. (CO5)
- Q.26 Draw and explain the circuit diagram of single phase half wave controlled rectifier. (CO2)