

No. of Printed Pages : 4

188423

Roll No.

**Level 3, 2nd Sem / DVOC (Ref. & Air Cond., Medical
Imaging Tech., Auto Servicing, ITM, PT, SD,
AMT, FP, EMS)**

Subject : Basic Electronics

Time : 2 Hrs.

M.M. : 50

SECTION-A

Note: Multiple Choice questions. All questions are compulsory. (5x1=5)

Q.1 What is the charge of an electron?

- a) Positive b) Negative
- c) neutral d) none of the above

Q.2 Which component is used for rectification?

- a) resistor b) diode
- c) inductor d) capacitor

Q.3 What is the primary function of a capacitor?

- a) store charge b) generate current
- c) regulate voltage d) convert ac to dc

Q.4 In a PN junction diode, the depletion layer is formed due to :

- a) movement of electrons
- b) movement of holes
- c) combination of electrons and holes
- d) external voltage application

Q.5 Which of the following is a unidirectional device?

- a) resistor b) inductor
- c) diode d) transformer

SECTION-B

Note: Objective type questions. All questions are compulsory. (5x1=5)

Q.6 Define the Ohm's law.

Q.7 What is the full form of CRO?

Q.8 What is a semiconductor?

Q.9 Name two types of transistors.

Q.10 What is the function of a zener diode?

SECTION-C

Note: Short answer type questions. Attempt any six questions out of Eight questions. (6x5=30)

Q.11 Differentiate between AC and DC current.

Q.12 What are the applications of a PN junction diode?

Q.13 Define intrinsic and extrinsic semiconductors.

Q.14 Explain the working of a transistor in CE mode.

Q.15 What are the differences between CB, CE, and CC transistor configurations?

Q.16 What is the significance of the depletion layer in a diode?

Q.17 Explain the working of a simple rectifier circuit.

Q.18 What is the difference between a conductor and a semiconductor?

SECTION-D

Note: Long answer type questions. Attempt any one questions out of two questions. (1x10=10)

Q.19 Explain in detail the working of a Bipolar Junction Transistor (BJT) and its characteristics.

Q.20 Describe the operation of a full-wave bridge rectifier with a neat circuit diagram.