

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x8=16)

- Q.23 Explain two stage RC coupled amplifier with its frequency response and advantages .
- Q.24 Explain the construction and working of complementary symmetry push pull amplifier with its advantages.
- Q.25 Explain working of operational amplifier as
- a) Adder
 - b) Integrator

No. of Printed Pages : 4

Roll No.

221034/181031/171031

/121031/031031

3rd Sem / ECE, ECE (For Speech and Hearing Impaired), Eltx, Mecatronics, Med. Eltx, Power Eltx, Elect. Eltx. Engg.

Subject : Electronic Devices and Circuits- II/ Electronics Devices and Circuits / Analog Eltx - II

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple choice questions. All questions are compulsory (6x1=6)

- Q.1 The voltage gain is practically expressed in_____
- a) ampere
 - b) db
 - c) volt
 - d) watt
- Q.2 Which power amplifier has highest collector efficiency.
- a) class A
 - b) class B
 - c) class C
 - d) None
- Q.3 The voltage gain of emitter follower is
- a) one
 - b) two
 - c) three
 - d) none

- Q.4 Which of the following is not an LC oscillator?
- a) crystal b) hartley
- c) colpitts d) tuned
- Q.5 Monostable multivibrator has _____ stable states.
- a) 1 b) 2
- c) infinity d) 0
- Q.6 Op-Amp is abbreviated as _____
- a) Operational amplitude
- b) Operational amplifiers
- c) Operand amplifier
- d) none

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (6x1=6)

- Q.7 If a three stage amplifier has individual stage gains of 10db, 5db and 10db; then the total gain in db is _____
- Q.8 _____ amplifier is used to increase the voltage level of weak signal.
- Q.9 Expand CMRR.

(2) 221034/181031/171031
/121031/031031

- Q.10 _____ feedback is used in oscillator. (Positive/Negative)
- Q.11 An Ideal op-amp has _____ voltage gain.
- Q.12 555 IC has _____ pins.

SECTION-C

Note: Short answer type questions. Attempt any eight questions out of ten questions. (8x4=32)

- Q.13 What is the need of multistage amplifier?
- Q.14 Differentiate between voltage and power amplifier.
- Q.15 Write a short note on heat sink.
- Q.16 Explain the working of single tuned voltage amplifier.
- Q.17 Explain the effect of negative feedback on gain and bandwidth of an amplifier.
- Q.18 Explain the working of Hartley oscillator.
- Q.19 Explain the barkhausen criterion for oscillations.
- Q.20 Define slew rate and CMRR.
- Q.21 Draw and explain the working of block diagram of IC 555 Timer.
- Q.22 Write a short note on Astable multivibrator.

(3) 221034/181031/171031
/121031/031031