

- Q.29 What do you understand by phase and phase difference in case of alternating quantities.
- Q.30 State and explain Kirchhoff's laws.
- Q.31 What is the relation between voltage, current and resistance of an electric circuit.
- Q.32 What is meant by self inductance and mutual inductance? Define the units in which each is measured.
- Q.33 State any five differences between A.C. and D.C.
- Q.34 Define admittance, susceptance and conductance and prove that in a parallel circuit $I = VY$.
- Q.35 Explain two wattmeter method to measure power in a 3-phase unbalanced load.

SECTION-D

- Note:** Long answer type questions. Attempt any two questions out of three questions. (2x10=20)
- Q.36 State and explain the points to be observed in order to maintain a lead acid cell in good working condition. How would you make sure that the battery has been completely charged and discharged.
- Q.37 A current carrying conductor experiences a force when placed in a magnetic field. Name two factors that affect the magnitude of the force.
- Q.38 Write short note on any two:
- 3-phase balanced and unbalanced circuits
 - importance of power factor
 - energy stored in a magnetic field

No. of Printed Pages : 4

120926

Roll No.

2nd Sem / Elect, Power Stat. Engg., Elect. & Eltx Engg., Fire Tech & Safety

Subject:- Fundamentals of Electrical Engineering

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 Which of the following statements is incorrect?
- Resistance is a passive element
 - inductor is a passive element
 - Current source is passive element
 - voltage source is an active element
- Q.2 The specific resistance of a conductor depends upon
- length of conductor
 - nature of conductor material
 - diameter of conductor
 - all (a), (b) and (c)
- Q.3 The specific gravity of acid is checked with the help of
- hydrometer
 - hygrometer
 - lactometer
 - cell tester
- Q.4 Which of the following is unit of inductance?
- ohm
 - henry
 - ampere turns
 - webers/meter

- Q.5 The form factor will be
 a) 1.0 b) 1.100
 c) 1.1 d) 1.187
- Q.6 The statement, factor sum of all the e.m.f.'s in any closed circuits is zero is associated with
 a) Faraday's law b) ohm's law
 c) kirchhoff's law d) coulomb's law
- Q.7 In two wattmeter method of measuring power in balance 3-phase circuit, if the readings of two wattmeters are equal but opposite in sign, then the power factor of the load is
 a) Unity b) 1/2
 c) zero d) 0.5
- Q.8 The power factor of series resonant circuit is
 a) zero b) unity
 c) 0.5 d) always lagging
- Q.9 Average emf of nickel & cadmium cell is
 a) 1.0 V b) 1.2 V
 c) 1.8 V d) 2.0 V
- Q.10 Killowatt-hour (kwh) is a unit of
 a) current b) power
 c) energy d) resistance

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 What are primary cell?
 Q.12 Draw delta connection.
 Q.13 What is EMF?

(2)

120926

- Q.14 Frequency of DC IS _____.
- Q.15 The resistance of a magnetic circuit is similar to _____ of an electric circuit.
- Q.16 State Lenz's law.
- Q.17 Power factor = active power / _____?
- Q.18 A wattmeter is used to measured _____
- Q.19 Define magnetic flux?
- Q.20 The Thevenin voltage is the _____

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 How do you defined the resistance of a conductor? What are the factors upon which it depends?
- Q.22 State and explain Norton's theorem.
- Q.23 What precautions would you observe in maintenance of a battery?
- Q.24 What is the similarity between an electric circuit and a magnetic circuit.
- Q.25 State Faraday's laws of electromagnetic induction. Mention two practical applications of this law.
- Q.26 In an a.c system, define the following:
 a) amplitude b) cycle
 c) time period d) frequency
 e) phase difference
- Q.27 Prove that in a pure resistive circuit, the power consumed by it is $E_{r.m.s} * I_{r.m.s}$
- Q.28 Compare star and delta systems of three phase connections.

(3)

120926