

- Q.28 Draw block diagram of 555 timers?
 Q.29 Explain Heat sink in power amplifiers.
 Q.30 Explain working of Astable multivibrator.
 Q.31 Explain working of IC voltage regulator.
 Q.32 Explain positive Feedback in amplifiers.
 Q.33 Explain transistors as a switch.
 Q.34 Explain the uses of multivibrator circuits.
 Q.35 Explain PIN diagram of IC 741

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain single ended tuned voltage amplifier.
 Q.37 Explain Emitter Follower Amplifier circuit and its applications.
 Q.38 Explain RC as differentiator and as Integrator circuit.

No. of Printed Pages : 4 180933/170933/120943
 Roll No.

3rd Sem / Electrical, Power Station Engg., Elect. & Eltx. Engg. Subject:- Electronics II

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 A common device which can work as an electronic switch is_____
- | | |
|---------------|--------------|
| a) Transistor | b) Amplifier |
| c) Alternator | d) Repeater |
- Q.2 An ideal OP Amp has_____ bandwidth
- | | |
|-------|-------------|
| a) 0 | b) Infinite |
| c) 10 | d) 100 |
- Q.3 The monostable mutivibrator has only_____ stable state
- | | |
|--------|---------|
| a) One | b) Two |
| c) No | d) None |
- Q.4 An oscillator use_____ feedback
- | | |
|-------------|-------------|
| a) Negative | b) Positive |
| c) Both | d) None |

Q.5 Push Pull amplifier use

- a) Class A b) Class B
- c) Class C d) Class ABC

Q.6 Integrator circuit is

- a) Loss pass filter b) High pass filter
- c) Clamper circuit d) None

Q.7 A schmitt trigger uses _____ feedback to generate square wave

- a) Positive b) Negative
- c) Current series d) None

Q.8 555 timer consists of _____

- a) 8 pin b) 5 pin
- c) 7 pin d) 9 pin

Q.9 In class A Amplifier, operating point is located at _____

- a) Centre of load line b) Near saturation
- c) Cut of point d) None

Q.10 The output waveform of 555 timer is _____

- a) Sinusoidal b) Triangular
- c) Rectangular d) Elliptical

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

Q.11 What is Heat Sink?

Q.12 A 555 timer is 8 pin IC _____ (True/False)?

Q.13 For tuned circuit, Bandwidth = _____?

Q.14 What is series resonance.

Q.15 What is negative feedback.

Q.16 What is voltage amplifier?

Q.17 What is clipping circuit.

Q.18 The negative feedback reduces _____ in amplifier.

Q.19 Push pull amplifier uses class _____?

Q.20 The distortion is maximum in _____ type of power amplifiers.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

Q.21 Write the applications of tuned voltage amplifier?

Q.22 Write a brief note on Piezoelectric crystal.

Q.23 Explain in brief operation of Class B amplifier.

Q.24 Discuss the effect of negative feedback on gain, distortion and bandwidth.

Q.25 Explain Phase shift oscillator.

Q.26 Explain transistor as a switch.

Q.27 Define offset even voltages and current.