

- Q.25 What is an inverter? Write any three applications.
- Q.26 What is a chopper? Explain its different types.
- Q.27 Explain the working of a dual converter in detail.
- Q.28 Explain working of a single -phase cycloconverter using centre tapped transformer.
- Q.29 What is electric drive? Explain it with the help of block diagram of an electric drive system?
- Q.30 Explain the working of single phase half wave converter drive with waveforms.
- Q.31 What is UPS? Explain different types of UPS?
- Q.32 Discuss the basic idea of heat sink selection for SCRs. Why is it important?
- Q.33 What are the specifications and ratings of SCR? Explain in detail.
- Q.34 Discuss the concept of high voltage DC transmission. Why is it preferred in certain applications?
- Q.35 Write short note on “thyristor protection”.

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain the construction and working principle of TRIAC and DIAC with their V-I characteristics.
- Q.37 Explain the working principle and characteristics of UJT. How is it used as a relaxation oscillator?
- Q.38 Explain with the help of suitable diagram of an automatic battery charger.

No. of Printed Pages : 4

181043/171043

Roll No.

4th Sem / Eltx Subject:- Power Electronics

Time : 3Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 The primary function of an SCR in a power electronics circuit is as:
- Voltage control
 - Current control
 - Power amplification
 - Switching devices
- Q.2 Following is a type of inverter:
- Step-up inverter
 - Step-down inverter
 - Both a and b
 - None of these
- Q.3 The purpose of heat sink in an SCR circuit is:
- To increase voltage
 - To stabilize the power output
 - To dissipates heat and prevents damage
 - To regulate current
- Q.4 The primary purpose of cycloconverter is as:
- Converting AC to DC
 - Step-up conversion
 - Frequency conversion
 - Inverter operation

- Q.5 In an Off-line UPS system, power is supplied to the load:
- Only from the battery
 - From the inverter
 - Directly from the mains, with battery backup in case of power failure
 - None of above
- Q.6 UJT is widely used as:
- Oscillator
 - Pulse circuit
 - Both (a) and (b) above
 - None of above
- Q.7 A single phase full wave fully controlled bridge rectifier uses:
- 4 SCRs
 - 6 SCRs
 - 2 SCRs
 - 3 SCRs
- Q.8 A dual converter consists of two bridges out of which one works as :
- A rectifier the other as oscillator
 - A inverter the other as chopper
 - A inverter the other as frequency changer
 - A rectifier the other as inverter
- Q.9 A class-E chopper can operate in:
- 1st and 2nd quadrant
 - 2nd and 3rd quadrant
 - 1st and 4th quadrant
 - All the four quadrant
- Q.10 To turn off an SCR, it is necessary to reduce its current to less than:
- Trigger current
 - Holding current
 - Break over current
 - None of the above

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 UJT stands for: _____
- Q.12 The maximum efficiency of a half-wave controlled rectifier is: _____
- Q.13 An AC gate triggering is preferred over DC gate triggering. (True/False)
- Q.14 ADIAC is a unidirectional device. (True/False)
- Q.15 The output voltage of a controlled rectifier is maximum when firing angle is _____.
- Q.16 The duty cycle of a chopper is expressed as _____
- Q.17 SMF batteries are not costlier than lead acid batteries. (True/False)
- Q.18 Armature control method is used in dc motors to get speed _____ normal speed.
- Q.19 Step up chopper does not require forced commutation. (True/False)
- Q.20 LASCR stand for _____.

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Explain the working of SCR using its layer diagram.
- Q.22 Differentiate between holding current and latching current of a thyristor.
- Q.23 Differentiate between natural and forced commutation.
- Q.24 Explain the working of single phase full wave half controlled bridge rectifier.