

- Q.32 Explain charging of capacitors. (CO4)
 Q.33 Explain effect of temperature on resistance. (CO1)
 Q.34 Discuss various semiconductor in electronic components. (CO3)
 Q.35 Write operation of thermocouple. (CO2)

SECTION-D

Note: Long answer type questions. Attempt any two questions out of three questions. (2x10=20)

- Q.36 Explain the Faraday's law of electromagnetic induction. (CO6)
 Q.37 Discuss Analogy between electric and magnetic circuit. (CO5)
 Q.38 Explain Thevenin and superposition theorems in brief. (CO2)

No. of Printed Pages : 4
 Roll No.

187743/147743

4th Semester/ Aircraft Maintenance Subject : Elements of Electrical & Electronics Engineering -II

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Multiple choice questions. All questions are compulsory (10x1=10)

- Q.1 What is the frequency of AC generated in India?(CO1)
 a) 60hz b) 0hz
 c) 25hz d) 50hz
- Q.2 The algebraic sum of all the currents meeting at a junction is (CO2)
 a) 0 b) 1
 c) 2 d) 0.5
- Q.3 Ohm is the unit is (CO1)
 a) Power b) Energy
 c) Resistance d) None
- Q.4 The unit of current is _____. (CO2)
 a) Ampere b) KW
 c) KVA d) VOLT
- Q.5 Watt is the unit of (CO1)
 a) Force b) Flow
 c) Power d) Energy

- Q.6 The total work done in electric circuit is called (CO1)
 a) Energy b) Work
 c) Power d) Torque
- Q.7 What is the frequency of DC supply. (CO2)
 a) 60hz b) 0hz
 c) 25hz d) 50hz
- Q.8 The Neutral connection is available in _____ connection. (CO8)
 a) Star b) Delta
 c) Both is star and delta d) None of above
- Q.9 The phase difference between two phase in three phase connection is _____ degrees. (CO8)
 a) 120 b) 90
 c) 180 d) 360
- Q.10 The semiconductor element is (CO3)
 a) Copper b) Silicon
 c) Gold d) Wood

SECTION-B

Note: Objective/ Completion type questions. All questions are compulsory. (10x1=10)

- Q.11 Define electric power. (CO1)
 Q.12 Define conductor. (CO3)
 Q.13 Define KVL. (CO2)
 Q.14 Define photocell. (CO2)

- Q.15 Define capacitor. (CO4)
 Q.16 Define permeability. (CO5)
 Q.17 Define phase. (CO7)
 Q.18 Define reluctance. (CO5)
 Q.19 Define power factor. (CO7)
 Q.20 Define inductance. (CO6)

SECTION-C

Note: Short answer type questions. Attempt any twelve questions out of fifteen questions. (12x5=60)

- Q.21 Compare AC and DC supply. (CO7)
 Q.22 Explain the advantages of three phase supply. (CO8)
 Q.23 Discuss relationship between phase voltage & line voltage in star and delta connection with diagram. (CO8)
 Q.24 What is series resonance? (CO7)
 Q.25 Discuss about parallel plate capacitor. (CO4)
 Q.26 Write about self inductance. (CO6)
 Q.27 Explain energy stored in an inductance. (CO6)
 Q.28 Discuss about AC applied to pure Resistance. (CO7)
 Q.29 Explain about hysteresis losses. (CO5)
 Q.30 Explain the force applied on current carrying conductor. (CO6)
 Q.31 What do you understand by magnetism and demagnetism. (CO6)