

**Sem. 1 NEP
Electrical Engg.**

Sub : Principles of Electrical Engg.

Time : 3 Hrs.

M.M. : 60

SECTION-A

Note: Multiple Choice Questions. All Questions are compulsory. (6x1=6)

- Q.1 Electrical power is measured in : (CO-1)
 a) Weber b) Watt
 c) kWh d) Joule
- Q.2 The correct representation of ohm's law is : (CO-2)
 a) $V=I/R$ b) $I=R/V$
 c) $V=IR$ d) $I=VR$
- Q.3 _____ in magnetic circuit is equivalent to resistance in electric circuit: (CO-3)
 a) Flux b) Reluctance
 c) mmf d) Magnetic Field
- Q.4 When a metal is heated, its resistance: (CO-2)
 a) Increases b) Decreases
 c) Remains constant d) None of the above
- Q.5 A large B-H curve indicates _____ hysteresis loss: (CO-4)
 a) Higher b) Lower
 c) Zero d) No relation

Q.6 Electrolyte used in lead acid battery is : (CO-5)

- a) H_2SO_4 b) NaOH
 c) NaCl d) $CaSO_4$

Section-B

Note: Objective/Completion type questions. All questions are compulsory. (6x1=6)


- Q.7 Define electric current? (CO-1)
- Q.8 Expand mmf? (CO-3)
- Q.9 Define primary cell? (CO-5)
- Q.10 State Lenz's law? (CO-2)
- Q.11 Internal resistance of ideal voltage source is zero. (True/False) (CO-1)
- Q.12 Define electrolysis? (CO-2)

Section-C

Note: Short answer type Question. Attempt any eight questions out of ten Questions. (8x4=32)

- Q.13 What is Joule's law of electric heating? Explain? (CO-2)
- Q.14 Define resistance? List factors on which resistance of a material depends? (CO-1)
- Q.15 State and explain KCL and KVL with suitable diagram? (CO-2)

Q.16 Solve for i : (CO-2)

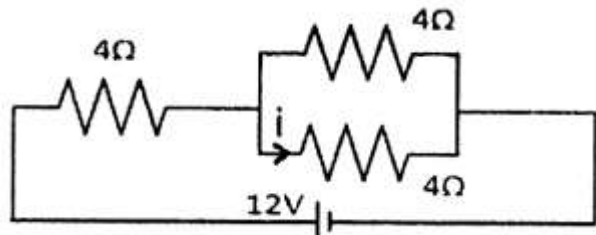

Q.17 Analyze analogous properties of an electric and magnetic circuit? (CO-3)

Q.18 Define: Reluctance and magnetic flux density. (CO-3)

Q.19 Explain Faraday's laws of electromagnetic induction. (CO-4)

Q.20 Write a note on eddy current and eddy current losses? (CO-4)

Q.21 How do we take care of lead acid batteries? (CO-5)

Q.22 State and explain Faradays law of electrolysis with suitable diagram? (CO-2)

Section-D

Note: Long answer questions. Attempt any two question out of three Questions. (2x8=16)

Q.23 Discuss important parts of lead acid battery with suitable diagram? Give function of each part? (CO-5)

Q.24 Define hysteresis (B-H) curve? Discuss its significance along with various terms associated with it? (CO-3)

Q.25 Explain star to delta conversion of a resistor network? Solve for R_1 , R_2 and R_3 : (CO-1)

