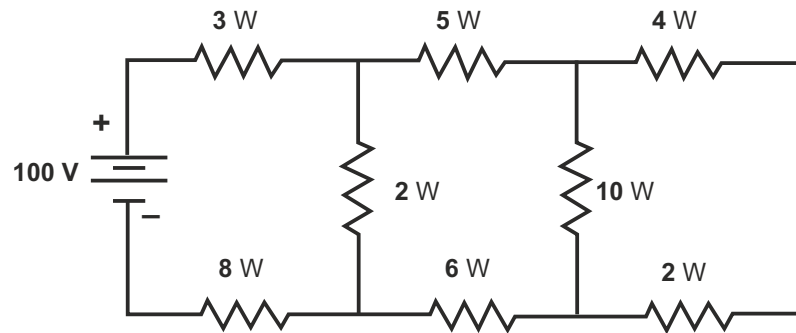


- Q.32 What is a maintenance free battery?
 Q.33 What are the various types of earthing?
 Q.34 What is a servo motor?
 Q.35 Write in brief about Semi-Conductors.

SECTION-D

Note: Long answer questions. Attempt any two questions out of three Questions. (2x10=20)

- Q.36 Find the current through each branch by network reduction technique.



- Q.37 What are the various applications of Single Phase and Three Phase Motors? Describe in detail.
 Q.38 A 10 Ohm resistor is connected in series of 230V 50 hz supply what is the
 a) Peak Voltage
 b) Current flowing and the power dissipated in the resistor
 c) If an Inductor $L=50$ mH is added to the circuit in series, what is the total impedance
 d) What is the current flowing in R-L circuit
 e) What is the power dissipated in AC circuit?

No. of Printed Pages : 4
 Roll No.

187734/147734

3rd Sem.

Branch : Aircraft Maintenance Engg.

Sub.: Elements of Electrical & Electronics Engineering-I

Time : 3 Hrs.

M.M. : 100

SECTION-A

Note: Multiple type Questions. All Questions are compulsory. (10x1=10)

- Q.1 For making measurement an ammeter is connected in
 a) Parallel b) Series
 c) Earthed d) None of the above
- Q.2 Primary winding of a transformer _____.
 a) It always a high voltage winding
 b) Is always a low voltage winding
 c) Could either be a low voltage or high voltage winding
 d) Cannot be determined
- Q.3 Lenz law shows
 a) Magnitude of the current
 b) Direction of the current
 c) Power factor
 d) None of these
- Q.4 Capacitor is used in
 a) AC circuits b) DC circuit
 c) Both d) Cannot say

- Q.5 Which winding has more number of turns?
- Low voltage winding
 - High voltage winding
 - Primary winding
 - Secondary winding
- Q.6 What is the number of positive plates in a battery cell?
- One more than the negative plates
 - Two less than the negative plates
 - One less than the negative plates
 - Two more than the negative plates
- Q.7 What is the phase difference between voltage and current?
- 90 Degree
 - 60 Degree
 - 120 Degree
 - Zero
- Q.8 In a star connected system the current flowing through the line is
- Greater than the phase current
 - Equal to the phase current
 - Lesser than the phase current
 - None of these
- Q.9 A 68W resistor is connected across the terminals of a 3V battery. The power dissipation of the resistor is
- 132mW
 - 13.2 mW
 - 22.6 mW
 - 226 mW
- Q.10 How much continuous current can be drawn from a 60Ah battery for 14h?
- 42.8A
 - 428A
 - 4.28A
 - 4.2A

(2) 187734/147734

SECTION-B

Note: Objective type questions. All questions are compulsory. (10x1=10)

- Q.11 What is the instrument used for measuring Voltage?
- Q.12 Where is advantage of AC use?
- Q.13 What is power Factor?
- Q.14 What earthing is done?
- Q.15 What are the characteristics of stepper motors?
- Q.16 What is the use of ELCB?
- Q.17 What type of motors are used to drive pumps?
- Q.18 What is a proof motor?
- Q.19 What do you mean by light fan circuit?
- Q.20 What is the use of isolation transformer?

SECTION-C

Note: Short answer type Questions. Attempt any twelve questions out of fifteen Questions. (12x5=60)

- Q.21 Where are maintenance free batteries used?
- Q.22 What is the difference between a neural and earth wire?
- Q.23 What are the applications of stepper motors?
- Q.24 What are the various parameters of AC power?
- Q.25 How voltage is measured?
- Q.26 What is EMF and how it is different from Voltage?
- Q.27 Derive the EMF equation of a transformer.
- Q.28 What are the various applications of electric power?
- Q.29 Write the relation between the line and phase value of voltage and current in a balanced star connected load?
- Q.30 What are various types of fuses?
- Q.31 A 400V is applied to three star connected identical impedances each consisting of a 30W resistance in series with 3W inductance reactance. Find line current.

(3) 187734/147734